



Schrodingers Box

First edition

2022

Advanced DIY Auto Diagnostics & Repair



Matt Bernstein

Ayman Kamar

Preface and Introduction

I would like to start right off the bat by letting you know- this book is actually the work of a viewer on my YouTube Channel named Dr. Ayman Kamar. Ayman is from Egypt, and English is pretty distanced from his primary language but somehow he still managed to put together the bulk of what you have in front of you. I didn't even know he was working on this project- he literally just presented a draft to me out of the blue one day and I didn't even know what to say.

As you can see, this book was a tremendous amount of work and you really have Ayman to thank for it. I only put together the introductions and some descriptions on the diagrams. This is really Ayman's creation and he wanted you to have it as a resource if you need quick refreshers while in the field as opposed to trying to search and view a relevant video from my YouTube channel or Paid Content channel www.schrodingersboxQM.com.

It is important to note that this book is intended as a supplement and review to my video content. You will definitely not be able to just pick up the book, read it cover to cover, and then be able to do advanced engine and electrical diagnostics. The

diagrams will look like hieroglyphics at best until you understand the concepts quite well. But if you can understand the diagrams and text that is a great indication you have a good comprehension of the material and the book can be used as a quick review or reference. There are links to the relevant videos for every chapter and it will be necessary to understand the video material to get the most out of the book.

This will be an evolving work in progress so if you identify any corrections that need to be made or would like to request specific content, just let me know and we'll see about implementing those in future editions.

Ayman and I really do hope you enjoy the book and find it useful in cementing your understanding of these complex concepts and greatly elevating your capabilities as an advanced DIY.

Best wishes,
Matt Bernstein – Schrodinger`s Box

Advanced DIY Auto Diagnostics & Repair

Contents

Preface and introduction	1
Automotive terms	5
1 Basic electrical for beginners	6
1.1 Open circuit	8
1.2 Closed circuit	9
1.3 Ohm`s Law	10
1.4 How to measure voltage	10
1.5 Circuits with load and resistance	14
1.6 Voltage drop test	15
1.7 Parallel Circuits	16
1.8 How to measure a current	19
1.9 Diagnosis problems in 3 wire Sensors circuit	21
1.10 Relays	26
1.11 Don`t blow you PCM	31
2 Wiring diagram tutorial	34
3 Engine sensors	38
3.1 Mass air flow sensor	38
3.2 Intake Air Temp Sensor	40
3.3 Throttle Position Sensor	41
3.4 Manifold Absolute Pressure Sensor	42
3.5 Oxygen up Stream Sensor	43
3.6 Air fuel ratio sensor	44
3.7 Knock Sensor	45
3.8 Engine coolant temperature sensor	47
3.9 Camshaft position sensor	
Crankshaft position sensor	48
4 Fuel trims	51
4.1 fuel injection system	51

4.2 Fuel trims defenitions	52
4.3 Relation between O2S1 & LTFT & STFT	53
4.5 Diagnosis by O2S1 & LTFT & STFT	55
5 Engine systems	57
5.1 Air Injection Reaction	57
5.2 The Evaporative Emission System	59
5.3 Fuel pressure regulator	62
5.4 Exhaust Gas Recirculation	64
5.5 The variable valve timing solenoid	66
5.6 Secondary Ignition Waveforms	71
5.7 Engine cooling system	75
5.8 Air Conditioning System	78



Schrodingers Box

AUTOMOTIVE TERMS

Engine Fuel System		CTS	Coolant temp. sensor
FPS	Fuel pressure sensor	ECT	Engine coolant temperature
LTFT	Long term fuel trim	AC	Air Conditioning System
STFT	Short term fuel trim	EVAP	The Evaporative Emission System
AFR	Air fuel ratio	COP	Coil- on - Plug Ignition System
FPR	Fuel pressure regulator	Basic electrical	
Engine Air Intake System		DVOM	Digital Volt Ohm Meter
IAT	Intake air temp. sensor	V	Voltage
IAC	Idle air control actuator (valve)	I	Current
MAF	Mass air flow sensor	R	Resistance
MAP	Manifold absolute pressure sensor	GND	Ground
TPAP	Throttle plate angular position	GRD	Ground
TPS	Throttle position sensor	V.	VOLTS
WOT	Wide open throttle	Amp.	Amperage (current measuring unit)
VVT	variable valve timing	Omh. Ω	Resistance measuring unit
Engine Exhaust system		T°	Temperature
EGR	Exhaust gas regulator	Diagnosis	
O2S1	Oxygen upstream sensor	TDC	top dead centre
O2S2	Oxygen downstream sensor	B1	Bank 1
ETS	Exhaust temp. sensor	B2	Bank 2
OL	OPEN LOOP	IGN.	Ignition
CL	CLOSED LOOP	IGN-SW	Ignition Switch
Engine Sensors & systems		DTC	diagnostic trouble code
PCM	Power train control module	psi	Pounds per square inch
ECM	Engine control module	PWM	Pulse-width modulation
CPS	Camshaft position sensor	RPM	revolutions per minute
CKPS	Crankshaft position sensor		
CMP	Camshaft position sensor		
CKP	Crankshaft position sensor		
KS	Knock sensor		

SECTION 1

BASIC ELECTRICAL FOR BEGINNERS

This is by far the most important chapter in the book. If you can master basic electrical concepts, you will far exceed even the capabilities of many professional auto mechanics because most people in general have a very hard time understanding electrical. I strongly urge you to do the best you can to understand not only the concepts but also to be able to do some of the math equations as well. Most people just skip over Ohm's Law and all the "math stuff" but mastering this will help you to achieve the ultimate mastery of electrical- the ability to "visualize" it as opposed to following it by memorization or mechanically like a flow chart.

It really helps to visualize basic electrical by analogizing it with water. While there are a few exceptions, 95% of the time thinking about the behavior of water flowing through hoses or how rivers flow will be pretty similar to how electricity works. This will allow you to take a complex concept like Ohm's Law: $V=IR$ (V)oltage equals (I)Amperage times (R)esistance and rather than just calculate it and follow whatever it says, you will be able to actually "see" it at work. In the case of a garden hose- the water faucet is the voltage- the starting pressure. You can imagine if you have good water pressure from the faucet and a really thin hose- we know water would shoot out of the end of the hose really far. This is because inside the thin hose we have high resistance which causes high pressure. But we also know that if you wanted to fill up a glass of water with this thin hose it would take an extra-long time because while the water shoots out impressively, there isn't actually all that much water coming out as opposed to if you just filled the glass right from the faucet without the hose. So we can "see" that increasing (R)esistance

reduces flow (I) amperage. We could also replace the thin hose with a much wider hose and fill a glass of water about the same as directly from the faucet but the water would hardly shoot out of the end of the hose because a wider hose has less resistance which increases the flow of water but pressure is reduced. You can imagine all kinds of combinations like this that would allow you to answer what would happen in various electrical situations. Why does a car with a bad battery not start? Well, it's because it's like having the faucet only turned on just a little bit and expecting it to operate a sprinkler. There isn't enough "pressure" and therefore both flow and resistance are reduced. What if the battery is good but there is a bad starter cable with lots of corrosion? The car still doesn't start but it's not for lack of pressure- remember pressure will be high to the starter motor because of the resistance, but there will be much less flow so just the same way the sprinkler would barely work if you used a really thin hose with it- we know the pressure is high because the hose is thin (increases resistance) but there isn't enough water flowing through the sprinkler to make it operate.

Please watch the basic electrical video links and then when looking at the diagrams in this book- see if it helps to think about water behavior to understand how variables impact electrical performance.

VIDEOS LINK

<https://schrodingersboxqm.com/basic-electrical-for-beginners-part-1/>

<https://schrodingersboxqm.com/basic-electrical-for-beginners-part-2/>

<https://schrodingersboxqm.com/basic-electrical-for-beginners-part-3/>

<https://schrodingersboxqm.com/basic-electrical-for-beginners-pt-4-dvoh-and-testlights/>




<https://schrodingersboxqm.com/basic-electrical-for-beginners-pt5-parallel-circuitscmf/>

<https://schrodingersboxqm.com/basic-electrical-for-beginners-pt6-applying-concepts/>

<https://schrodingersboxqm.com/basic-electrical-for-beginners-pt7-conclusion/>

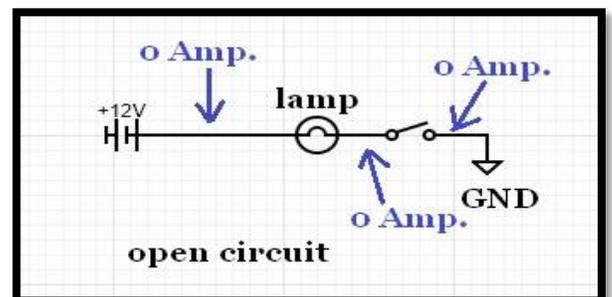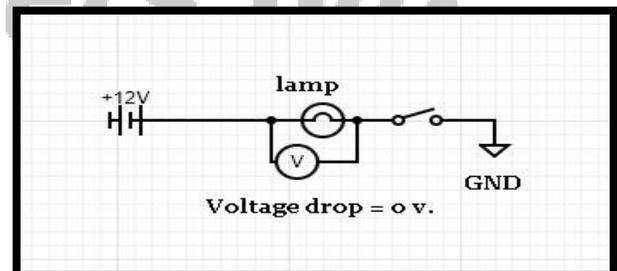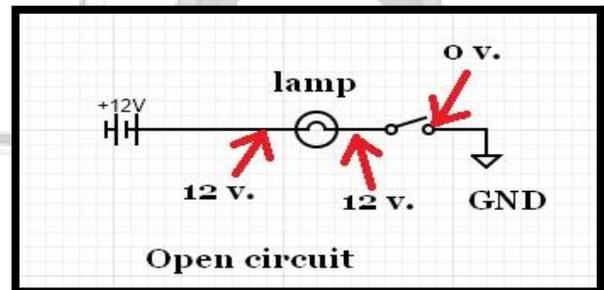
1.1 - Open circuit

- Any position BEFORE the open switch will equal source voltage because there is no current (flow). Think of water analogy- the open switch is “capping” the hose so all pressure is equal before the cap.
- When we calculate voltage drop across the load (the lamp) it is zero because there is no current with switch open.
- Current is zero Amps anywhere on circuit because there is no electrical flow with open switch. The lamp is not lit in any of these examples because switch is open—no flow.




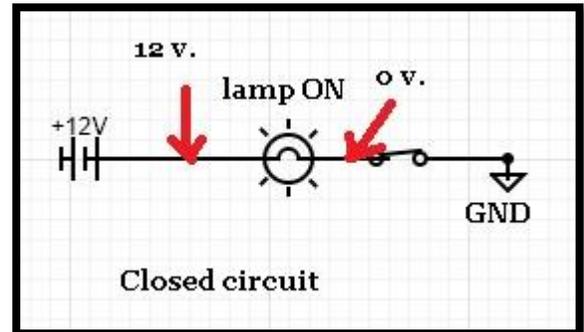1.2- Closed circuit (switch closed)


- The voltage BEFORE the load (lamp) equals source voltage but AFTER the load it is zero. The load uses all the voltage no matter its resistance. Lamp is lit because of switch closed causing flow.



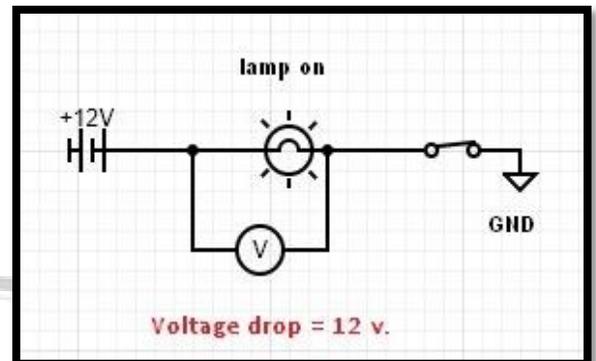- When we calculate voltage drop across the lamp, it is 12V because it is source voltage before the load and 0V after the load.



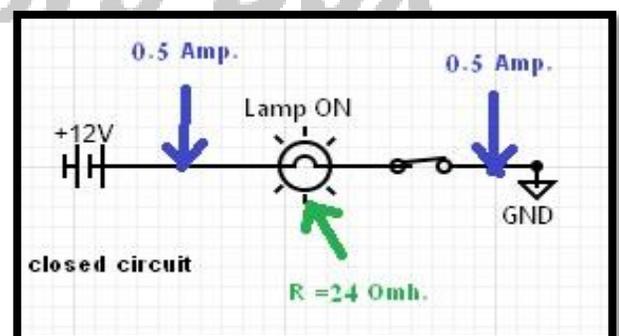- Unlike Voltage, CURRENT (amperage or I) will be the same across the ENTIRE circuit. Again, think of water analogy- water flow is same before or after a “pinch” in the hose. You can’t have water flow slower or faster within different points of a closed system- it’s all the same.



1.3- Ohm`s Law

V=Voltage I=Current (Amperage) R=Resistance


$$V = I * R$$

$$I = V / R$$

$$V = 12 \text{ V.}$$


$$R = 50 \Omega$$


$$I = 12 / 50 = 0.24 \text{ Amp.}$$

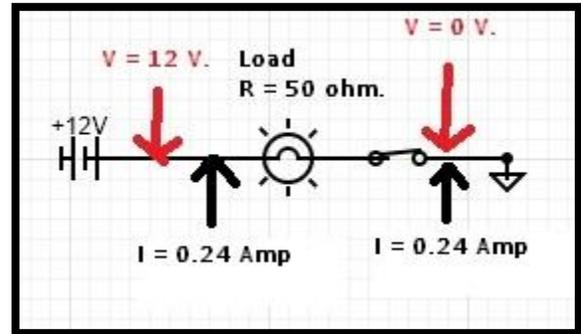


1.4- How to measure voltage

Example: fuel injector

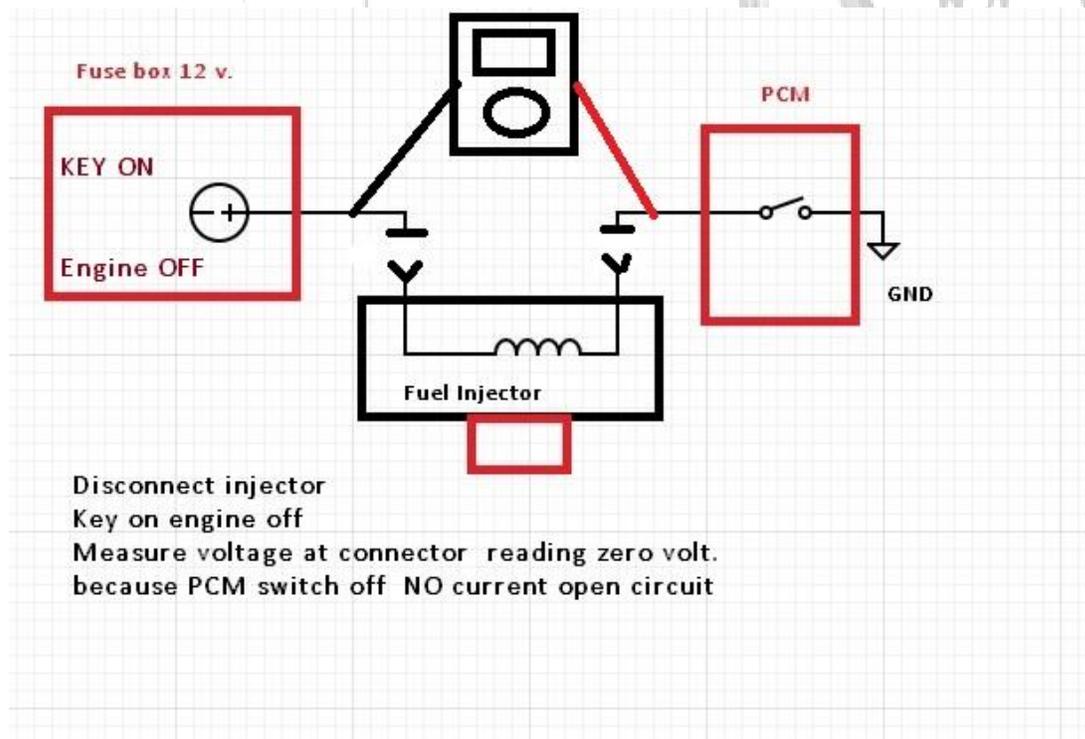


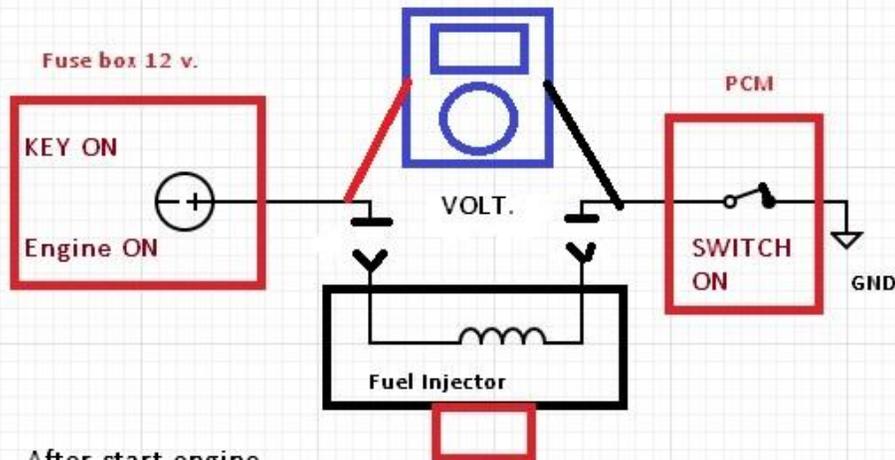

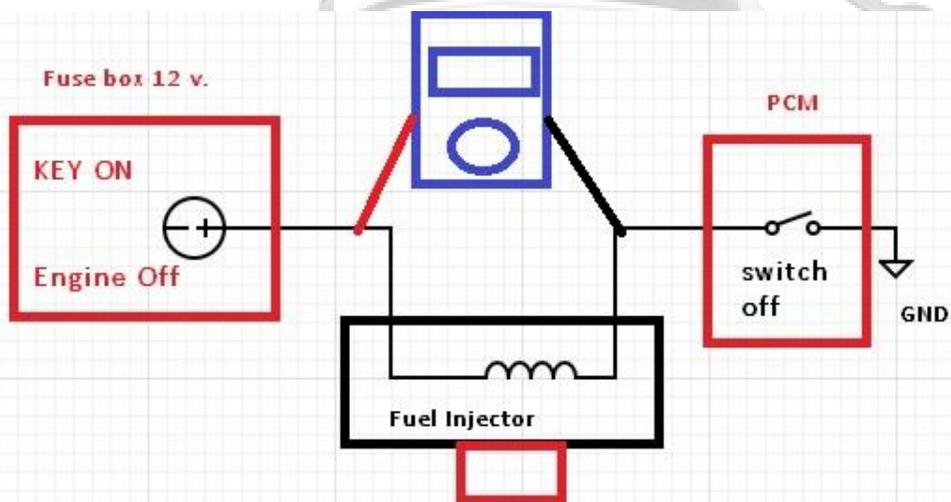
After start engine
PCM close the circuit
by measuring voltage
reading the average volt. about 6 volt
because PCM turns switch on & off periodically



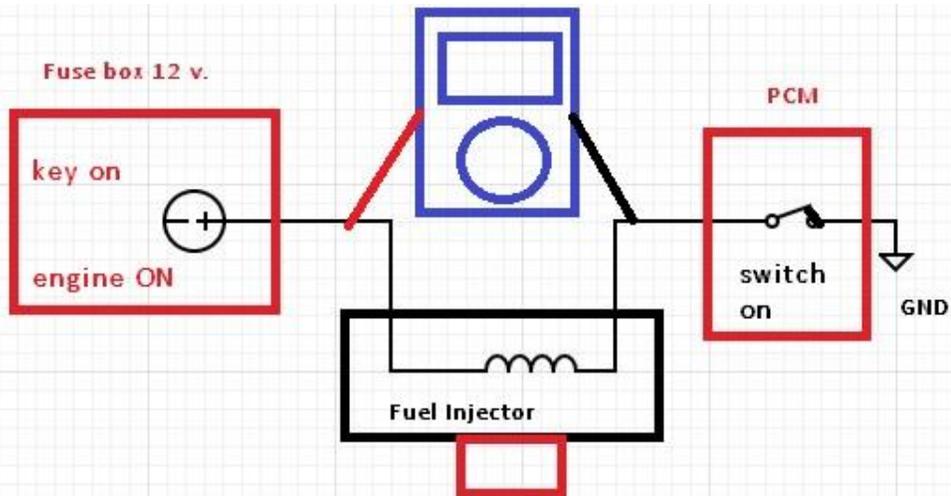
Connect injector
Key ON Engine off
Measuring voltage at connection
reading zero volt.
because PCM switch off No current open circuit



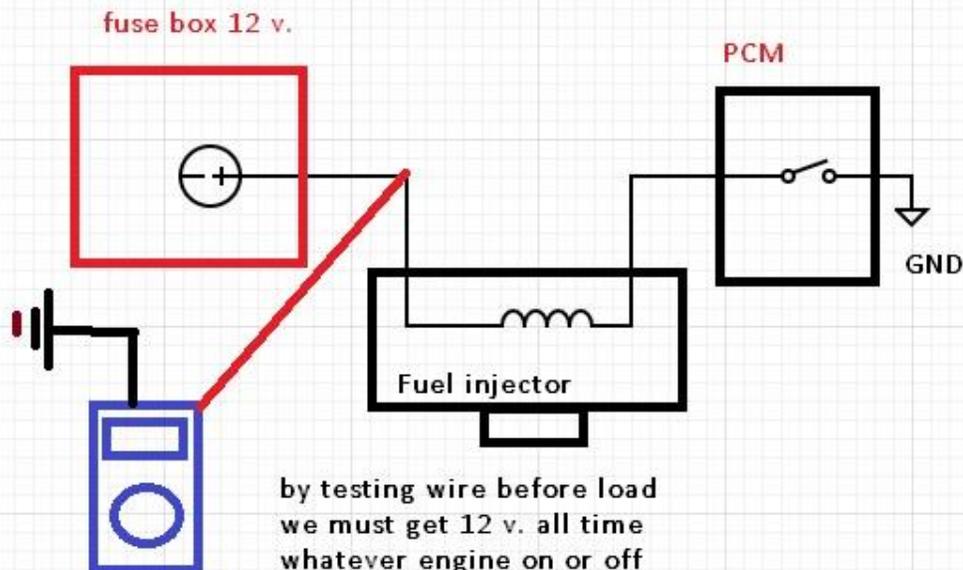
After starting engine
PCM close the circuit
by measuring voltage
Average volt. will be about 6 volt
because PCM turns switch on & off periodically



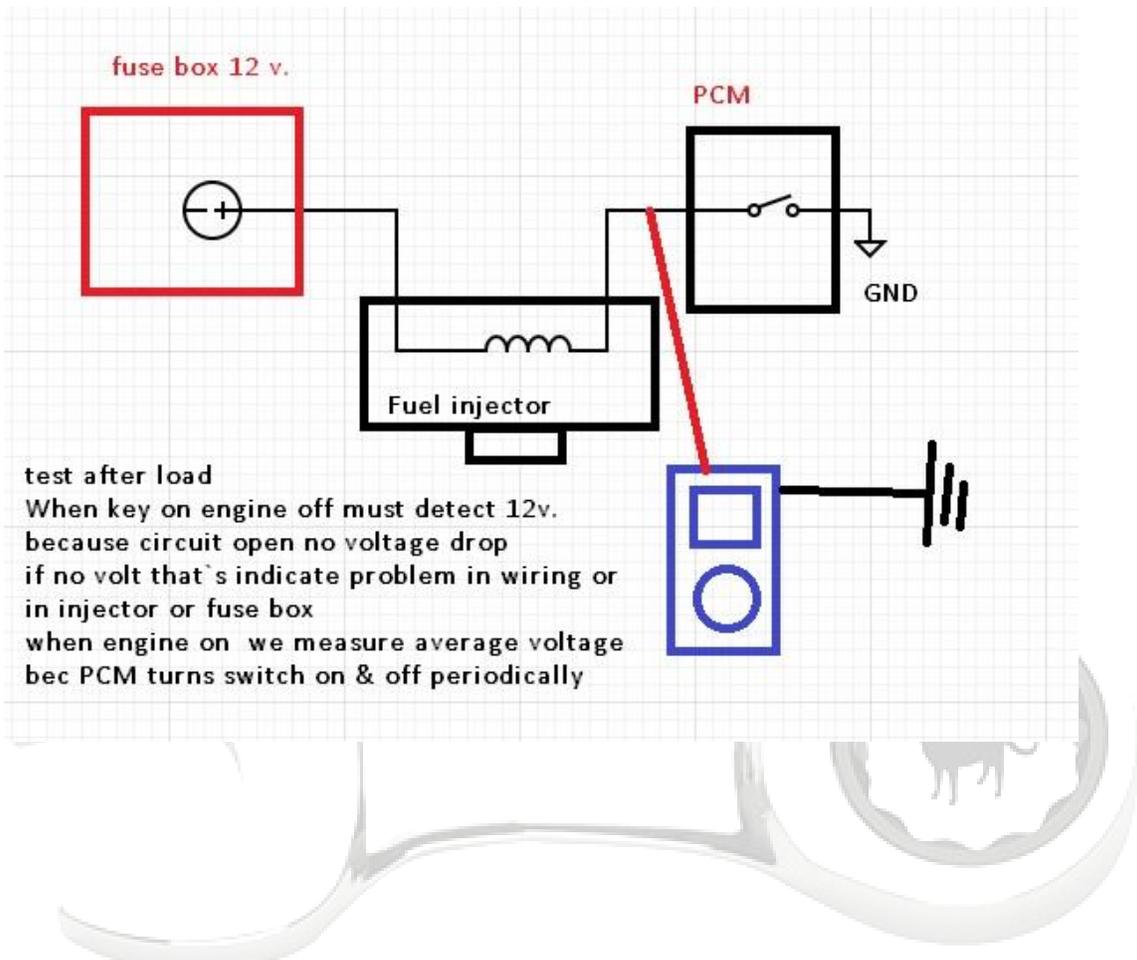by testing wire before load
we must get 12 v. all time
whatever engine on or off
as long key on
if we get zero volt that is indicate problem in wiring
or fuse box



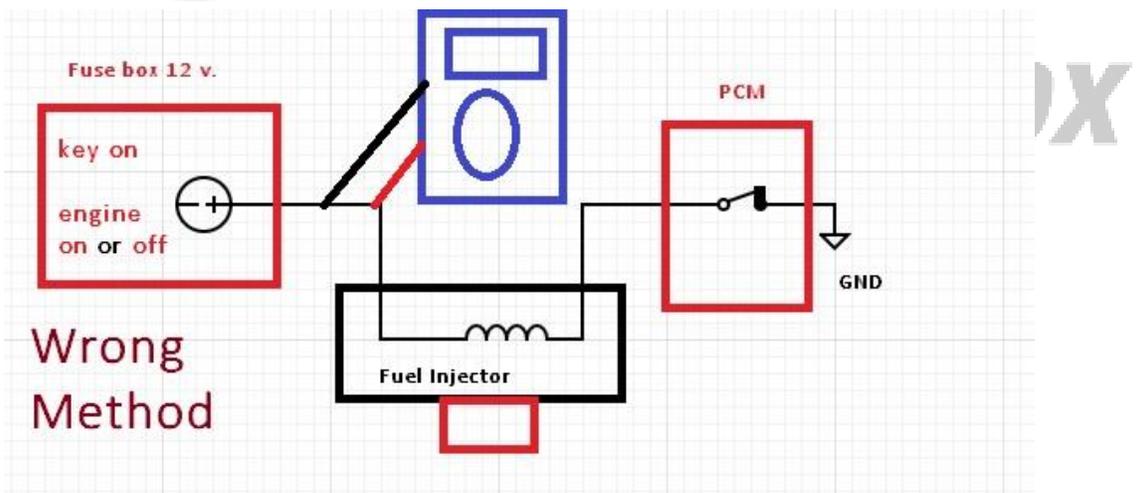test after load
 When key on engine off must detect 12v.
 because circuit open no voltage drop
 if no volt that's indicate problem in wiring or
 in injector or fuse box
 when engine on we measure average voltage bec
 PCM turns switch on & off periodically





Wrong Method

testing at harness by this way before load
 give us zero volt at any case because no voltage drop
 before load

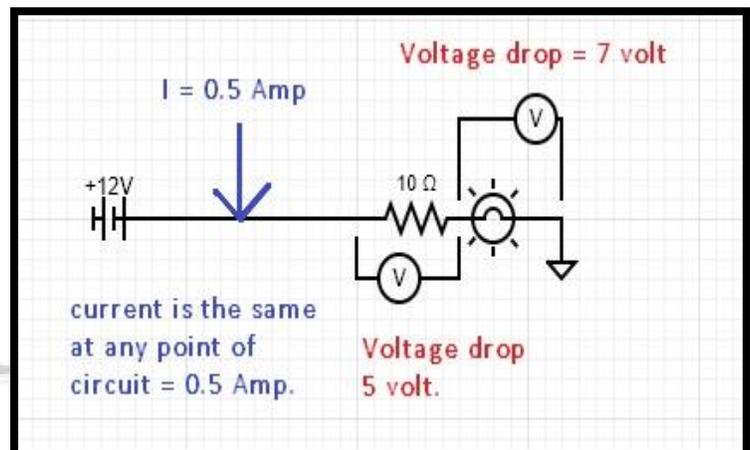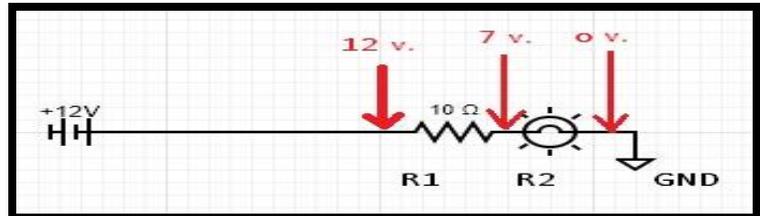1.5- CIRCUITS WITH LOAD AND RESISTANCE



Resistance before load

- $I = 0.5$ Amp
- $R_1 = 10 \Omega =$ RESISTANCE
- $R_2 = 14 \Omega =$ LOAD BULB
- **At R_1 RESISTANCE**
- $V = I R$
- $V = 0.5 \times 10 = 5$ VOLT
- Voltage drop = 5 volt
- Voltage after $R_1 = 7$ volt
- **At R_2 LOAD BULB**
- $V = I R$
- $V = 0.5 \times 14 = 7$ VOLT
- Voltage drop = 7 volt
- Voltage before $R_2 = 7$ volt
- Voltage after $R_2 = 0$ volt



Resistance after load

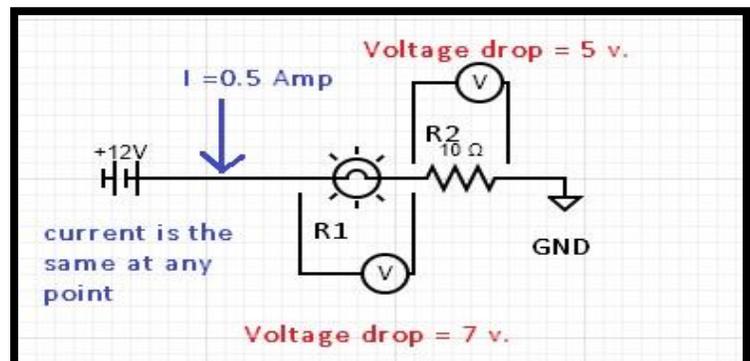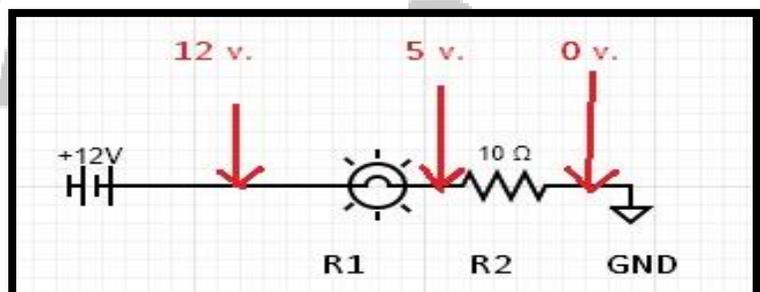- $I = 0.5$ Amp
- $R_1 = 14 \Omega =$ LOAD BULB
- $R_2 = 10 \Omega =$ RESISTANCE
- **At R_1 LOAD BULB**
- $V = I R$
- $V = 0.5 \times 14 = 7$ VOLT
- Voltage drop = 7 volt
- Voltage after $R_1 = 5$ volt
- **At R_2 RESISTANCE**
- $V = I R$
- $V = 0.5 \times 10 = 5$ VOLT
- Voltage drop = 5 volt
- Voltage before $R_2 = 5$ volt
- Voltage after $R_2 = 0$ volt





1.6- Voltage drop test

Video link

<https://youtu.be/DfLyh43iihM>


1 - FIRST WAY

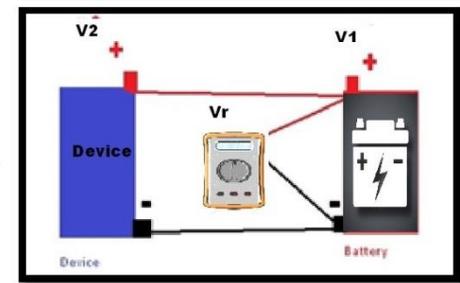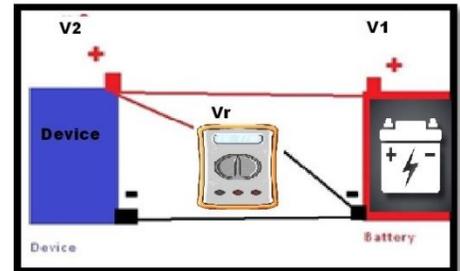- Check voltage at device positive terminal vs battery negative terminal (Figure 1) and subtract from battery voltage (Figure 2). Difference is voltage drop across positive cable. Remember- **DEVICE MUST BE OPERATING!** No current flow=no voltage drop.




2- SECOND WAY

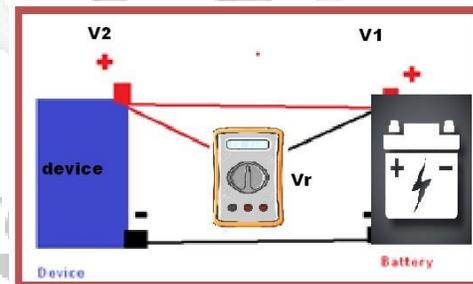- Connect +on device to +on source. This shows voltage drop on positive.
- If shows approximately zero, it means no voltage drop. Look for $>.6V$ on a starter motor.



Schrodinger's

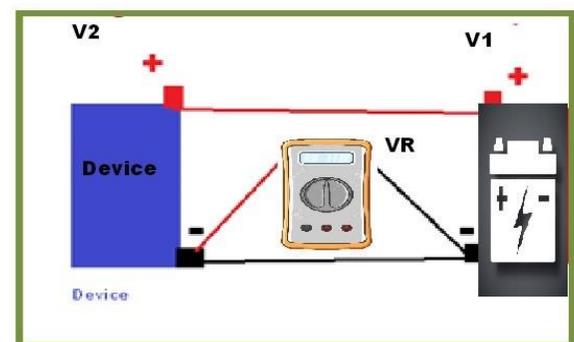- Repeat second way on Negative side to get voltage drop on the negative. Again- the circuit **MUST HAVE AMPERAGE FLOW!!** Voltage drop will show zero if there is no current flow **EVEN IF THERE IS HIGH RESISTANCE!!**



1.7- Parallel Circuits

(See basic electrical series on www.schrodingersboxQM.com for walkthrough)

- TWO PARALLEL RESISTANCES CIRCUIT

- example 1

- $R1=100\Omega$

- $R2=100\Omega$

- R_t = Total resistance

- $R_t = \frac{R1 \times R2}{R1 + R2}$


- $R_t = \frac{100 \times 100}{100 + 100} = 50\Omega$

- $V = I \times R$

- $I_t = \frac{V_t}{R_t} = \frac{12}{50} = 0.24 \text{ Amp.}$

- $I_1 = \frac{V_1}{R_1} = \frac{12}{100} = 0.12 \text{ Amp.}$

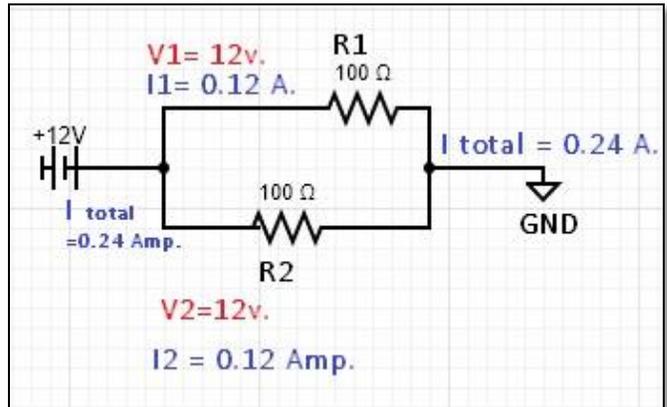- $I_2 = \frac{V_2}{R_2} = \frac{12}{100} = 0.12 \text{ Amp.}$



- example 2

- $R_t = \frac{R1 \times R2}{R1 + R2}$


- $R_t = \frac{100 \times 25}{100 + 25} = 20\Omega$

- $V = I \times R$


- $I_t = \frac{V_t}{R_t} = \frac{12}{20} = 0.6 \text{ Amp.}$

- $I_1 = \frac{V_1}{R_1} = \frac{12}{100} = 0.12 \text{ Amp.}$

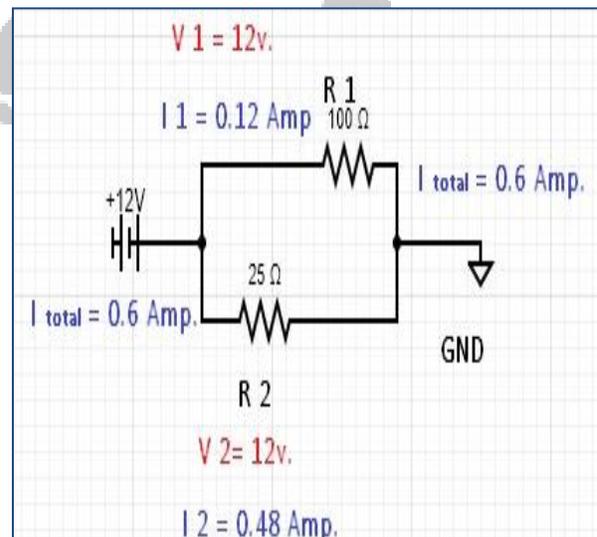- $I_2 = \frac{V_2}{R_2} = \frac{12}{25} = 0.48 \text{ Amp.}$



- Example 3

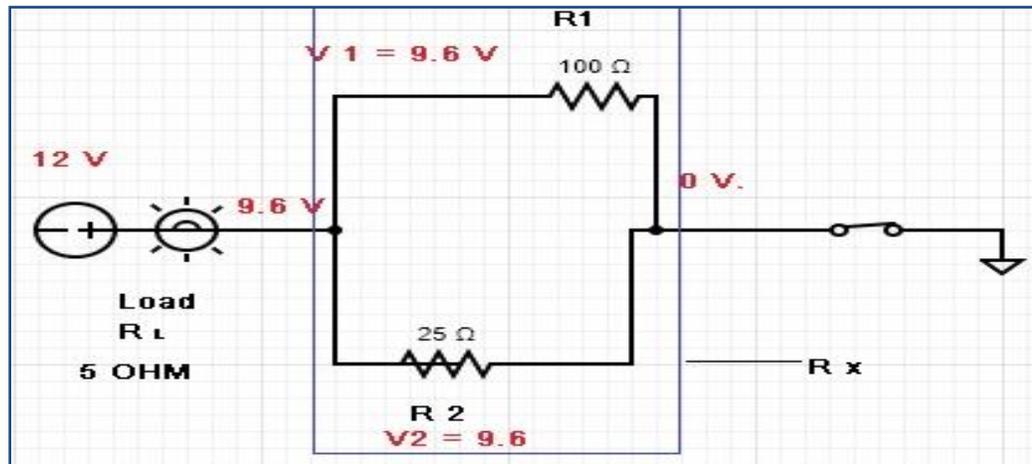

$$R_1 = 100\Omega$$

$$R_2 = 25\Omega$$


$$R_L = \text{Resistance at load} = 5\Omega$$

$$R_x = \text{Resistance at } R_1 \text{ \& } R_2 \text{ circuit}$$

Schrodinger's Box

- $R_x = \frac{R_1 \times R_2}{R_1 + R_2}$
- $R_x = \frac{100 \times 25}{100 + 25} = 20\Omega$
- $R_t = R_L + R_x = 5 + 20 = 25\Omega$
- $I_t = \frac{V_t}{R_t} = \frac{12}{25} = 0.48 \text{ Amp}$
- Voltage drop at load = $I \times R = 0.48 \times 5 = 2.4 \text{ V.}$
- $I_L = \frac{V_L}{R_L} = \frac{2.4}{5} = 0.48 \text{ Amp}$
- $I_1 = \frac{V_1}{R_1} = \frac{9.6}{100} = 0.096 \text{ Amp.}$
- $I_2 = \frac{V_2}{R_2} = \frac{9.6}{25} = 0.384 \text{ Amp.}$
- $I_x = I_1 + I_2 = 0.096 + 0.384 = 0.48 \text{ Amp}$

- THREE PARALLEL RESISTANCES CIRCUIT

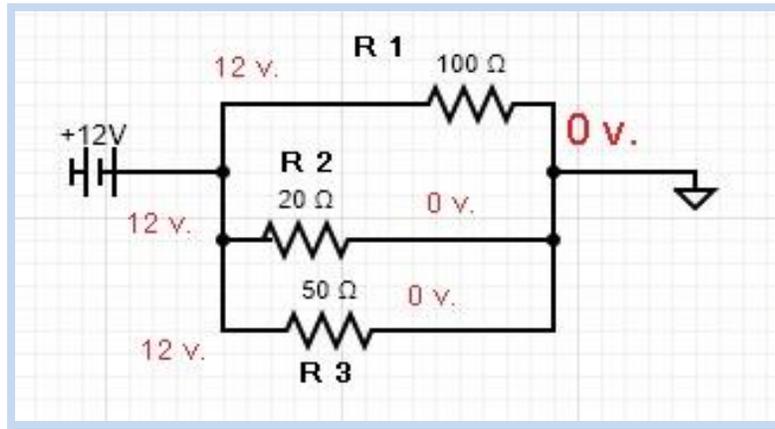

- $\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{?} \dots \dots$

- $\frac{1}{R_t} = \frac{1}{100} + \frac{1}{20} + \frac{1}{50} = 12.5 \Omega$

- $I_1 = \frac{V_1}{R_1} = \frac{12}{100} = 0.12 \text{ Amp.}$

- $I_2 = \frac{V_2}{R_2} = \frac{12}{20} = 0.6 \text{ Amp.}$

- $I_3 = \frac{V_3}{R_3} = \frac{12}{50} = 0.24 \text{ Amp.}$

- $I_t = \frac{V_t}{R_t} = \frac{12}{12.5} = 0.96 \text{ Amp}$

$$V = I R$$

$$R_t = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{?} \dots \dots$$

1.8 – How to measure current using a basic DVOM.


• Attention :

If you are not familiar with all basics for car electricity, don't try to measure current in this way because wrong methods can damage your PCM!! It works by creating a “jumper” wire between point without a load!!




- Turn DVOM Meter to a suitable range of Amperage (green circle)
- Make sure to connect the probe in the specific position of measuring high amperage (red circle)
- After measuring don't forgets you return the probe to the default position to be able to make other measurements correctly without any damage



Correct Method

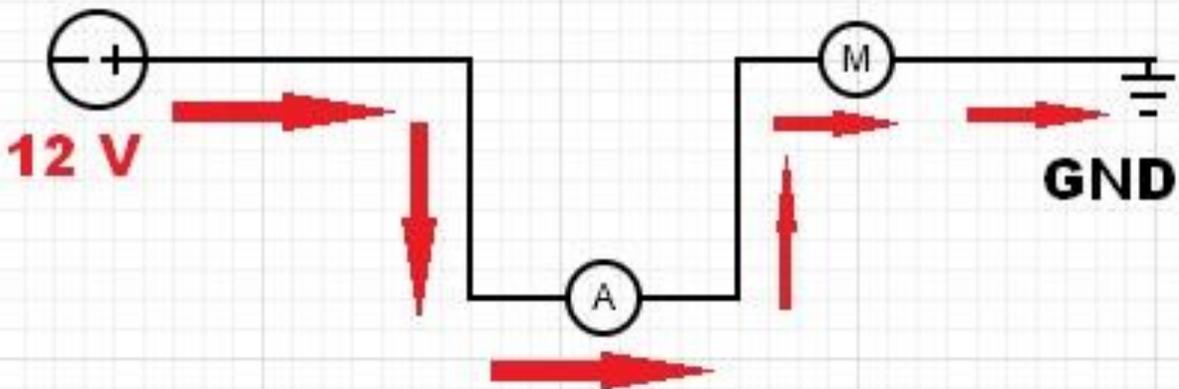

Here we have the Ammeter (A) correctly placed **IN SERIES** in the circuit. This can be done either before or after the load (M) because remember current flow is the same everywhere in the circuit, You could just as well connect between the (M) and the ground and get same result. “In Series” means you are “plugged into” **EITHER** the positive side **OR** the negative side **ONLY!** If you connect positive to negative you will have a short circuit!

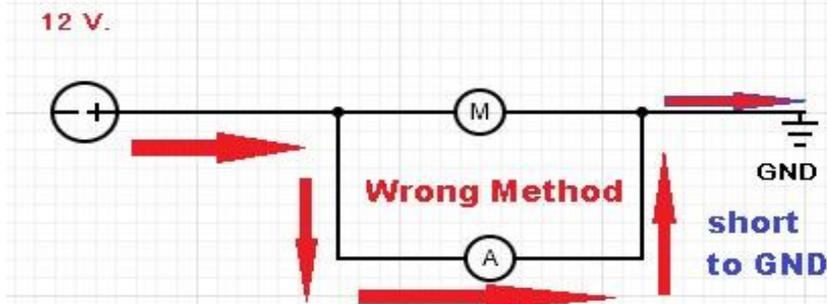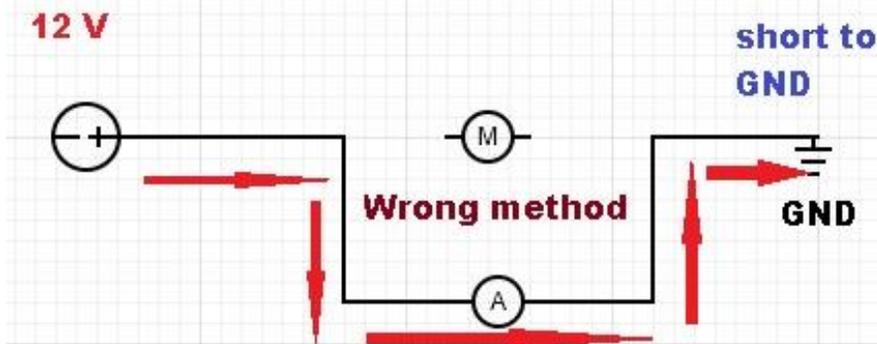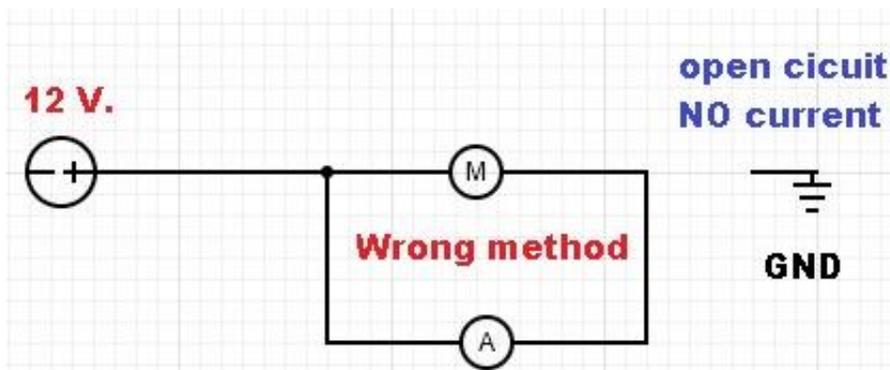



In the first wrong method we are trying to measure amperage on an open circuit. Reading will be zero because of no flow. The second and third diagrams are also wrong but also DANGEROUS!! We are basically “bypassing” the load with a jumper wire so we create a short circuit and can cause damage. Measuring VOLTAGE will not do this- but measuring AMPERAGE will!!!! This is also why its so important when measuring voltage to be certain your meter is not in amperage configuration!!!

1.9- DIAGNOSIS PROBLEMS IN 3 WIRE SENSORS CIRCUIT

A -NORMAL CIRCUIT



Can be tested by checking the voltage

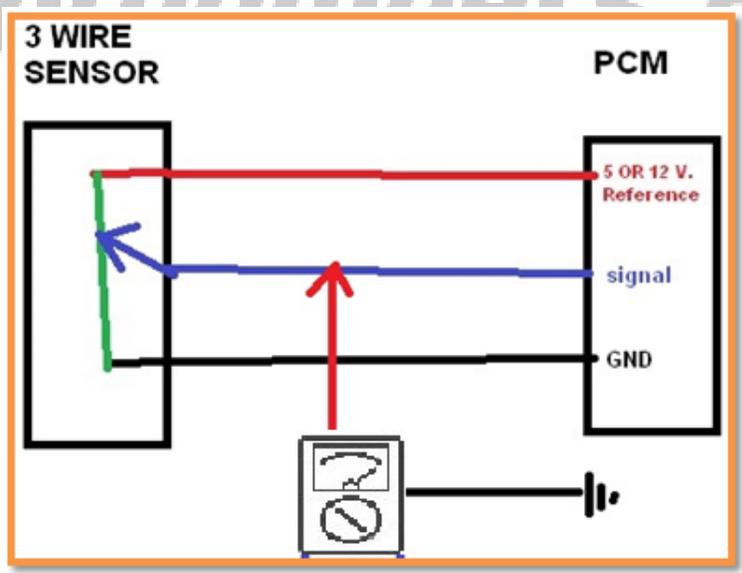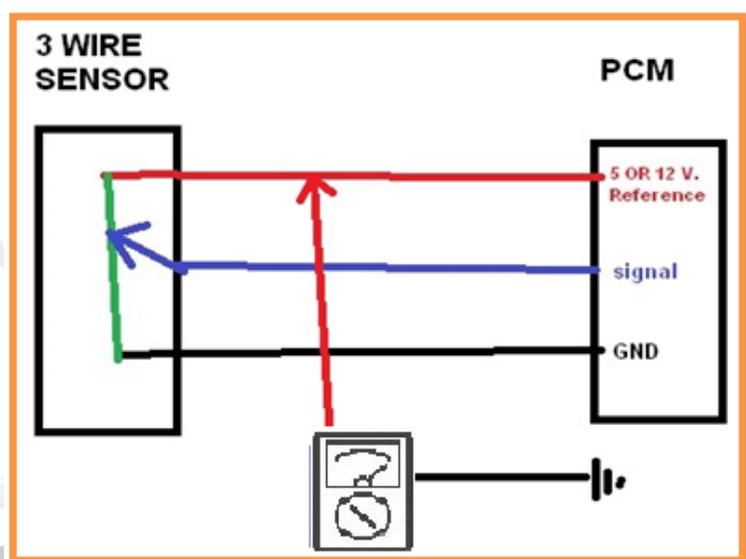- At reference = 5 v.
- At signal = 0.5 to 5 v.



B – OPEN CIRCUIT

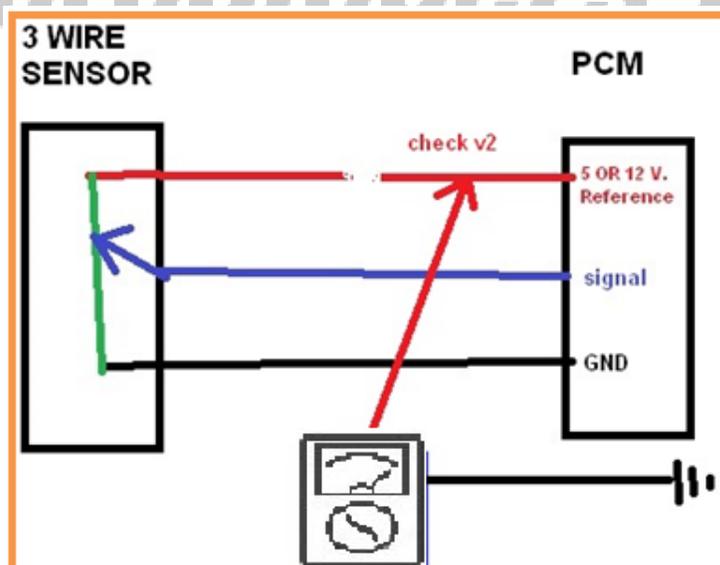
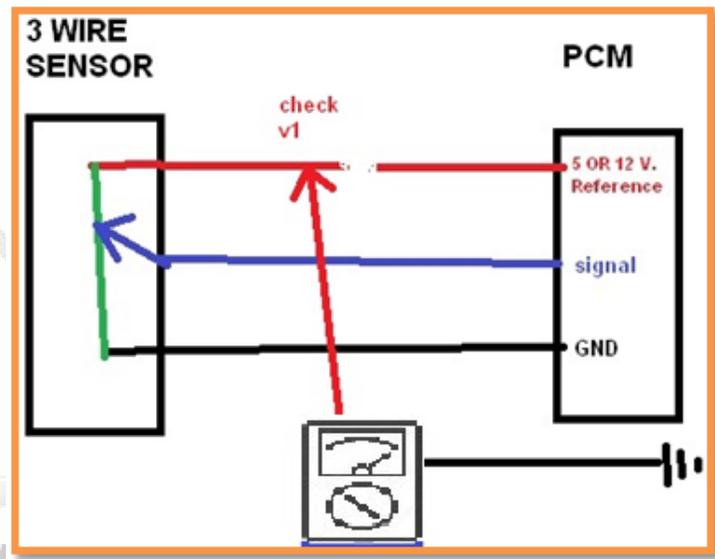
- Check connectivity at all sides
• Of connection wire from PCM to sensor
- Check voltage at 2 sides of reference = 5 v.
- Check voltage at 2 sides of signal $v1 = v2$



C – SHORT TO GROUND


- **METHOD 1 : disconnect sensor & PCM**
- Check cable connectivity to the ground
- If = O.L is normal no short
- If = sound it`s short

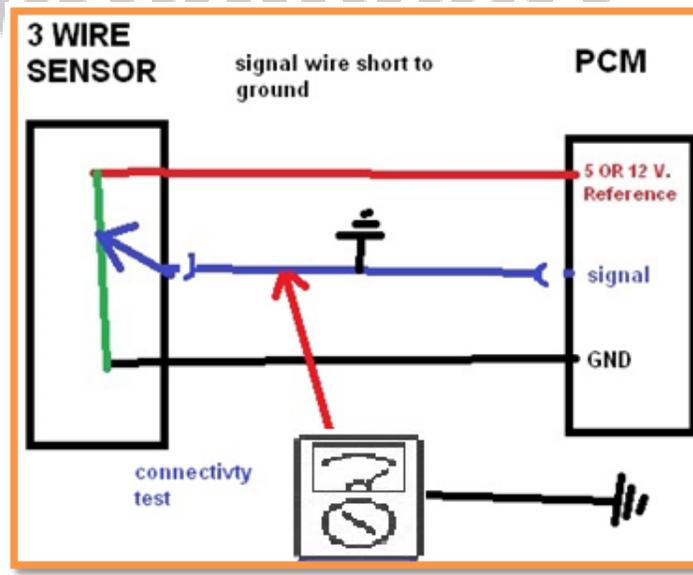
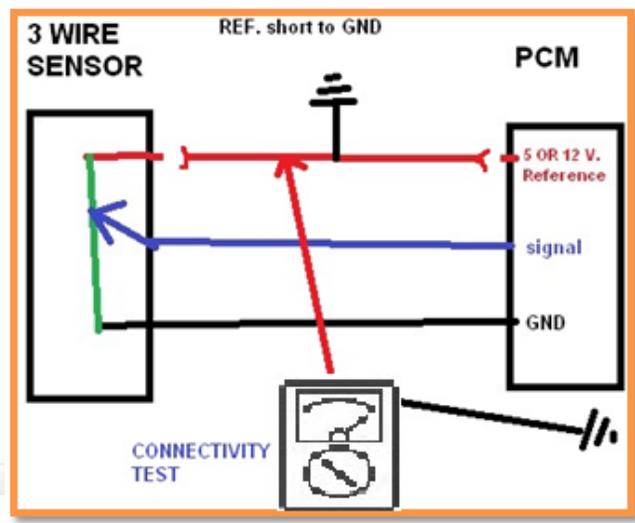
- **METHOD 2 : disconnect **sensor & PCM****
- Apply 12v. Test lamp to reference if the light on it`s a short
- Apply 12v. Test lamp to Signal if the light on it`s a short



D - UNDESIRABLE RESISTANCE (VOLTAGE DROP)

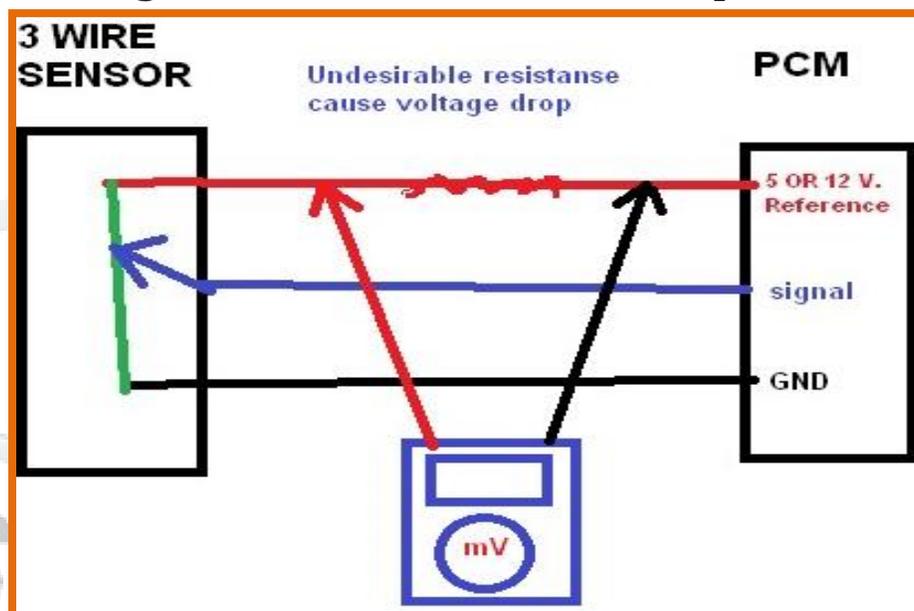- 1- Check voltage at both sides of the reference
IF $V1 = V2$ it's normal NO VOLT. DROP
- 2- Check voltage at both sides of the signal
IF $V1 = V2$ it's normal NO VOLT. DROP
- 3- Check Mille voltage at both sides of the ground cable
If voltage < 100 millivolt it's normal NO Volt. DROP
If voltage > 100 millivolt it's volt. drop



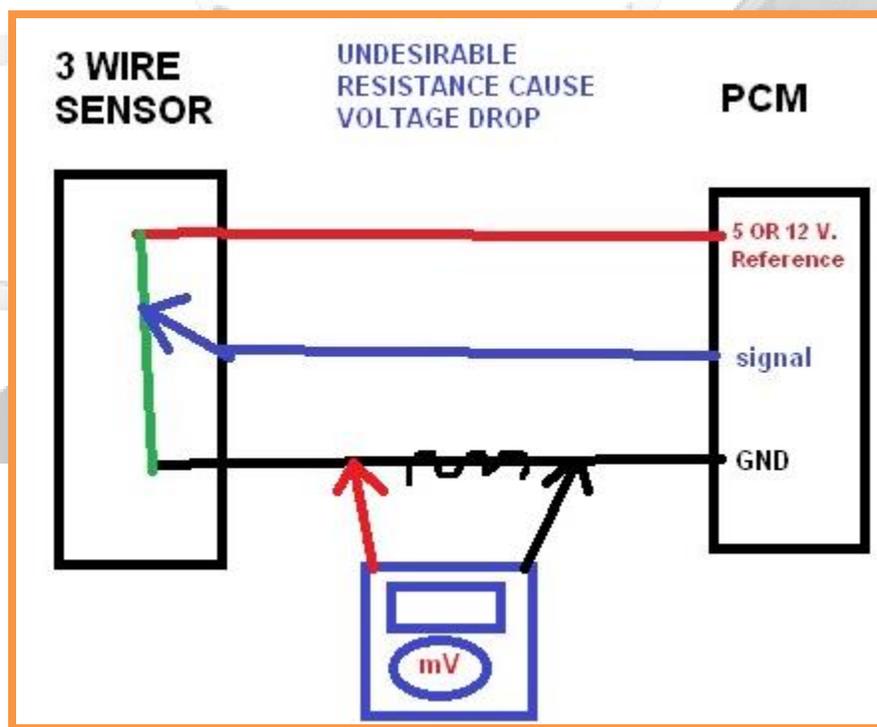
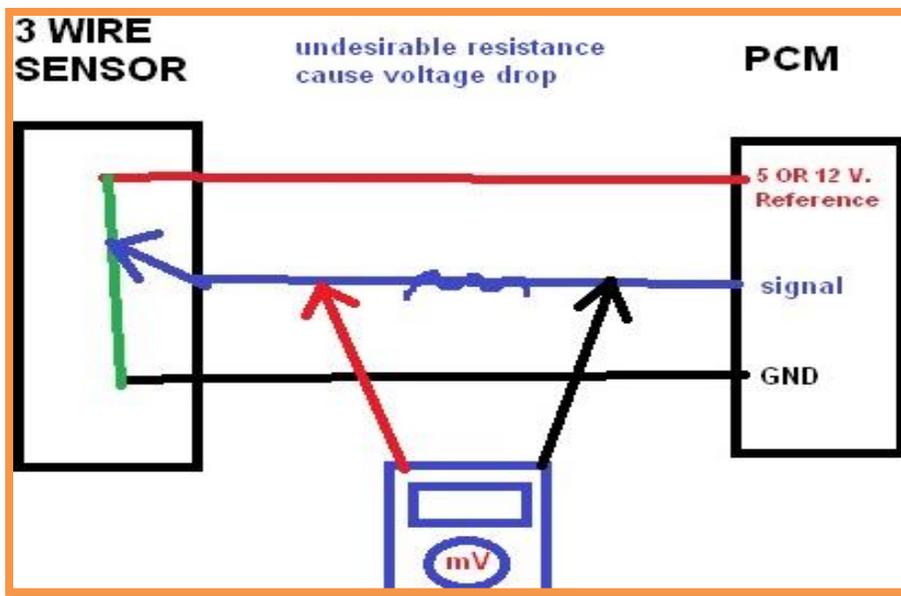


1.10- Relays



https://www.youtube.com/watch?v=Gg20X-FwGzg&t=28s&ab_channel=SchrodingersBox



https://www.youtube.com/watch?v=fxGZIBNTFPE&t=3s&ab_channel=SchrodingersBox



In a relay regardless of how many pins, there are essentially 2 sides- control and load. The idea is to allow a low current to be able to control a high current which is easier on a switch and also safer. The control side is the low voltage side that the operator controls with a switch- maybe a headlamp switch. This closes the control side circuit and operates a magnet inside the relay that magnetically pulls the high current switch to close and complete circuit to operate the load (headlamp device in this example). Additional pins basically put load to different parts of circuit.

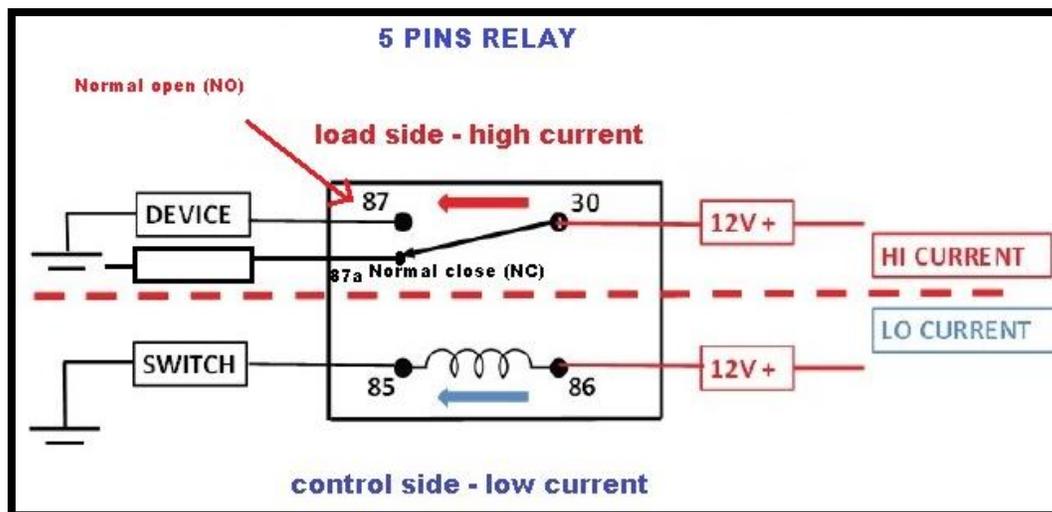
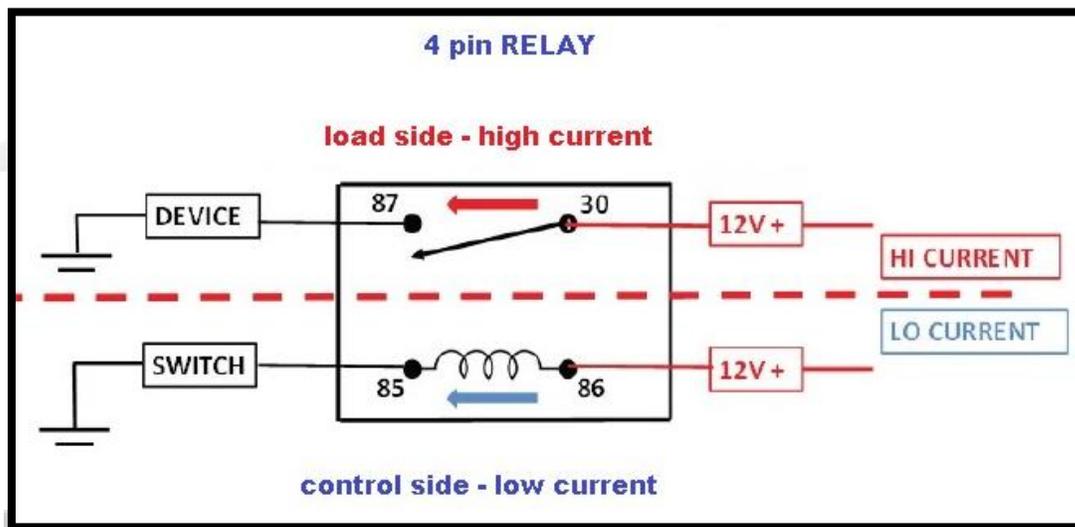


TESTING RELAYS

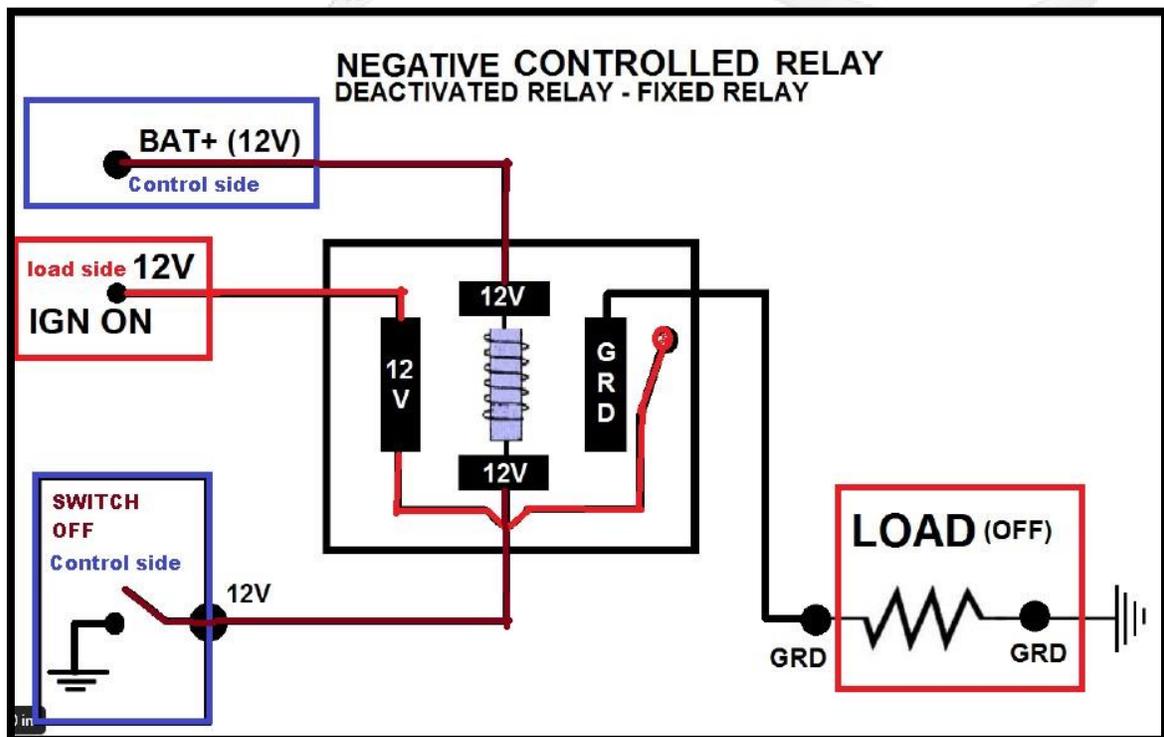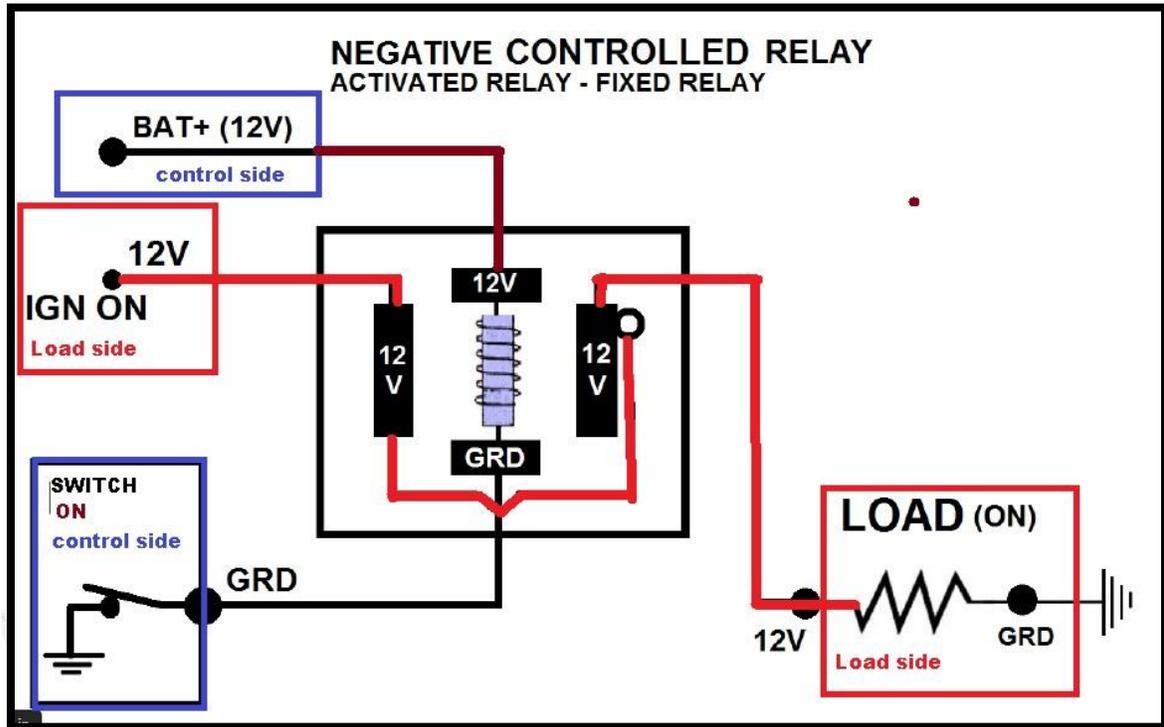

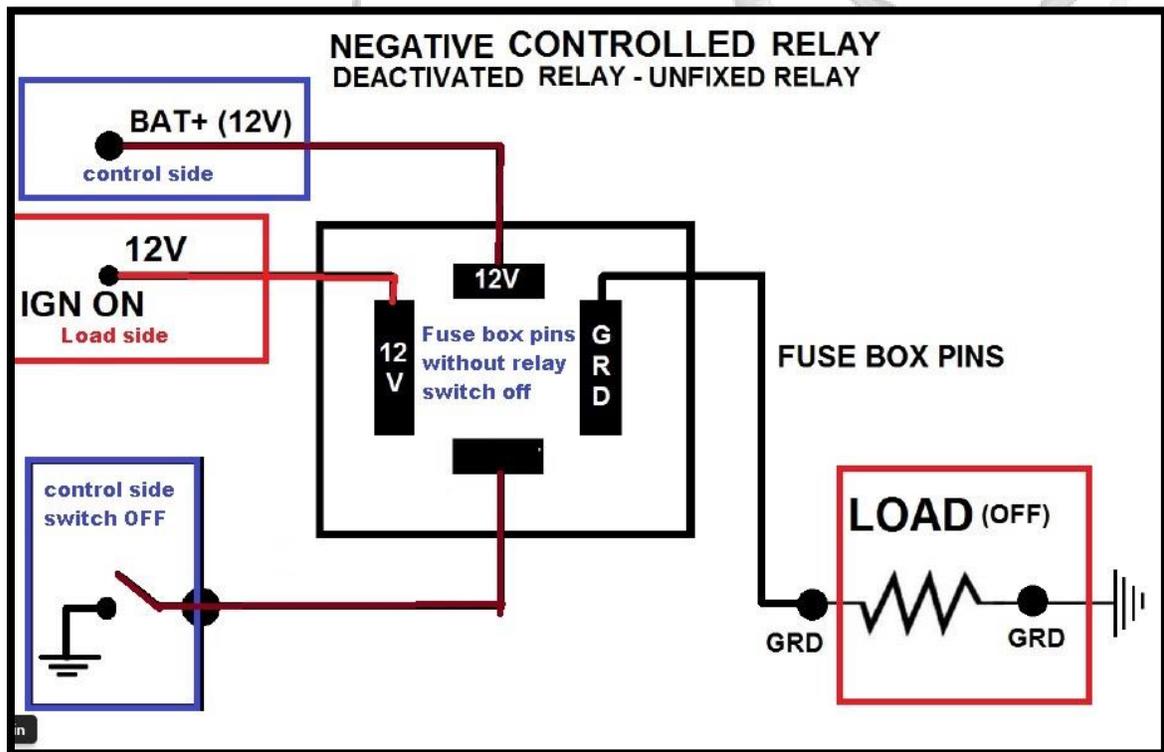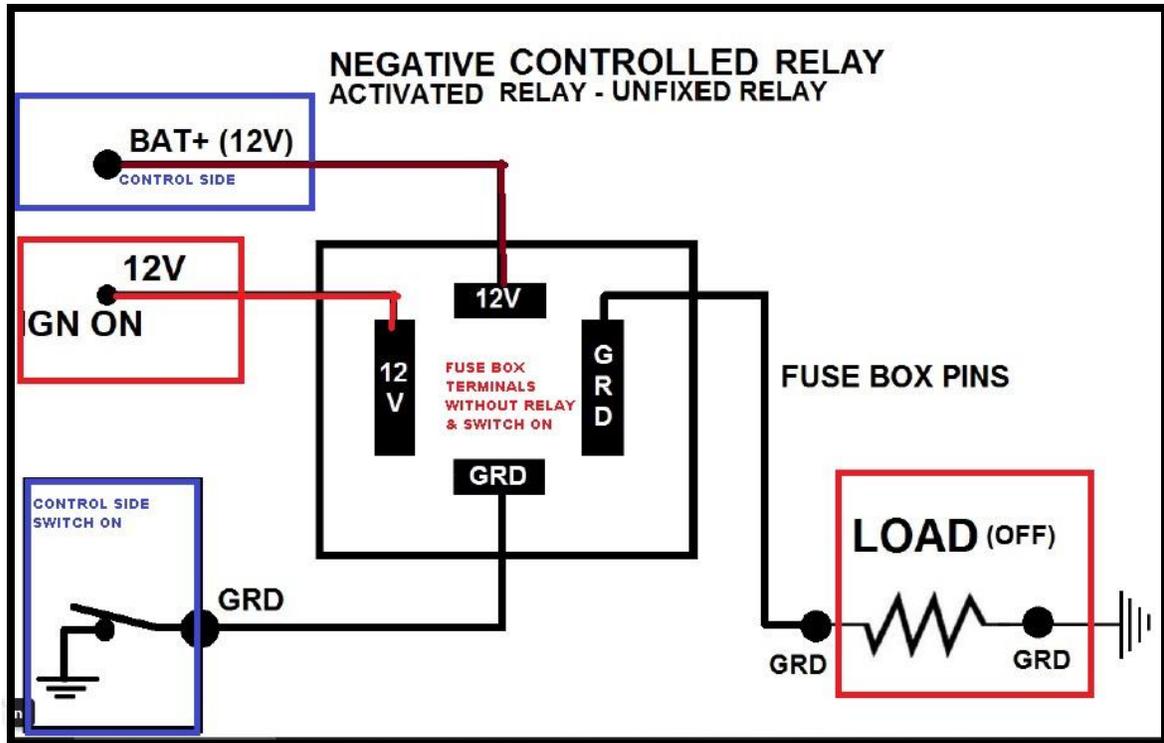

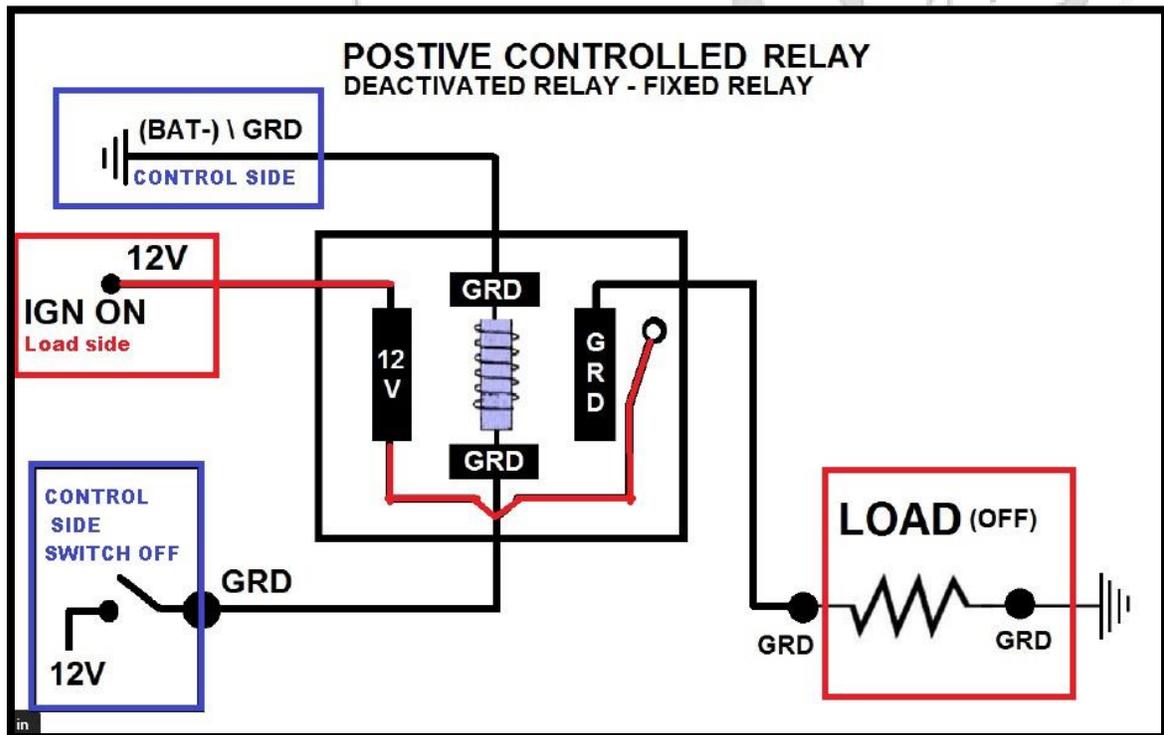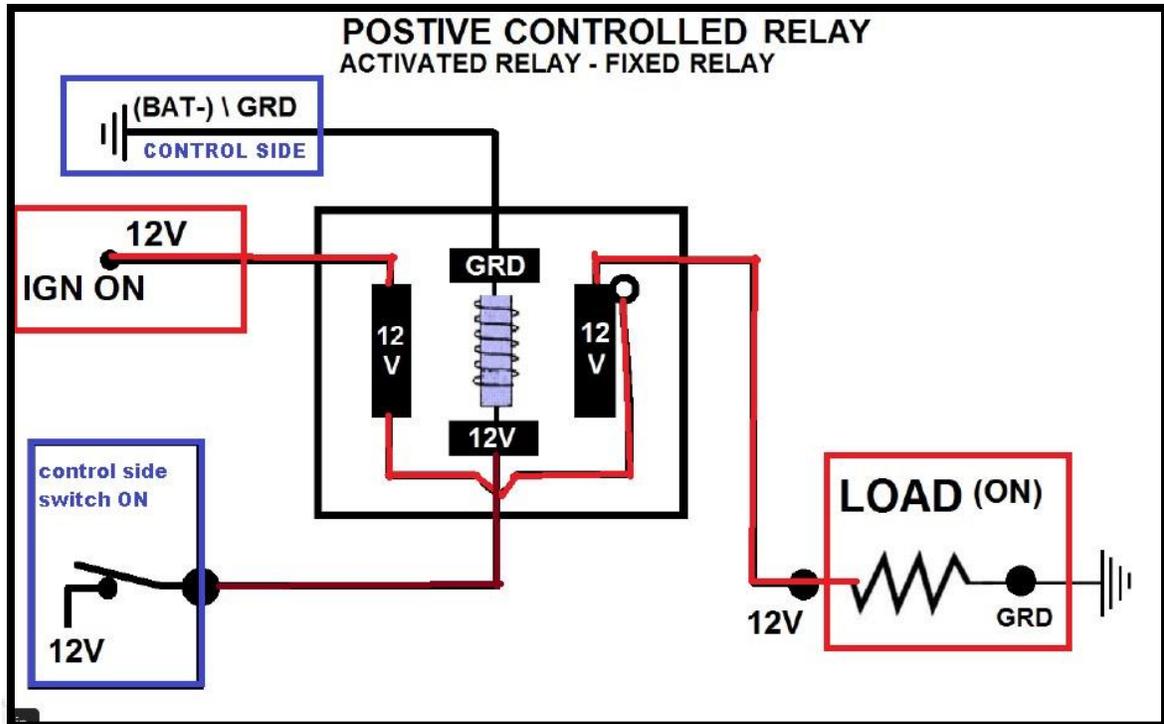

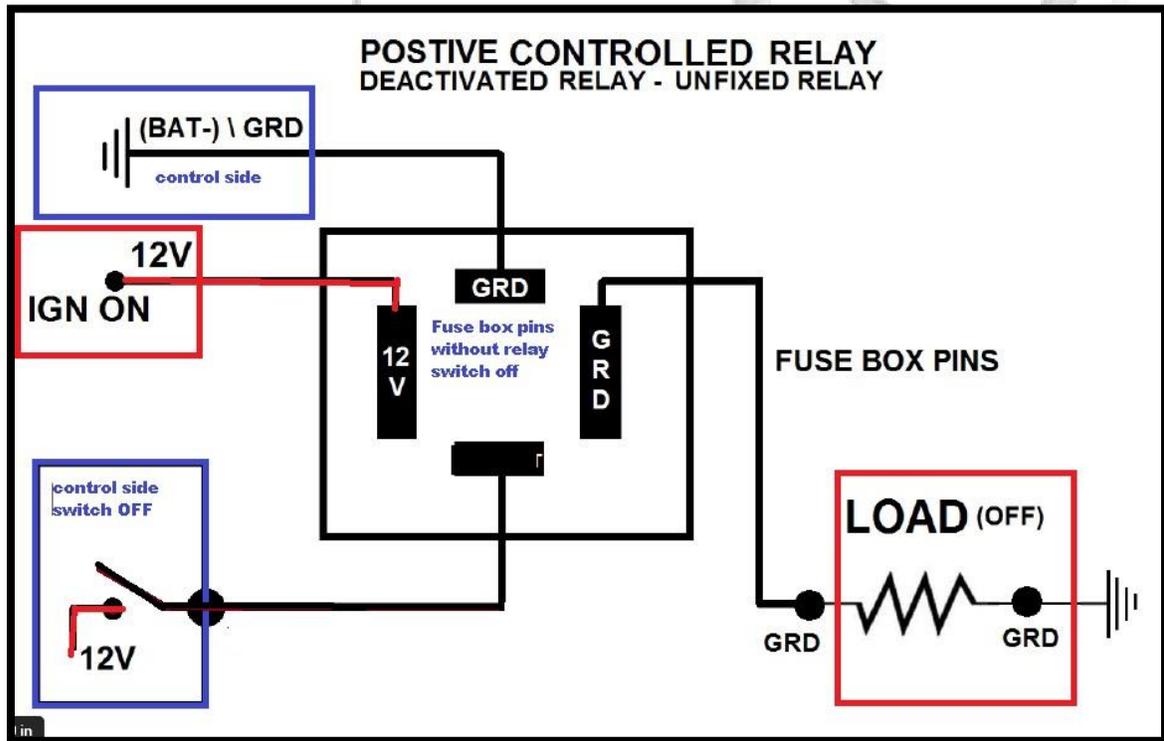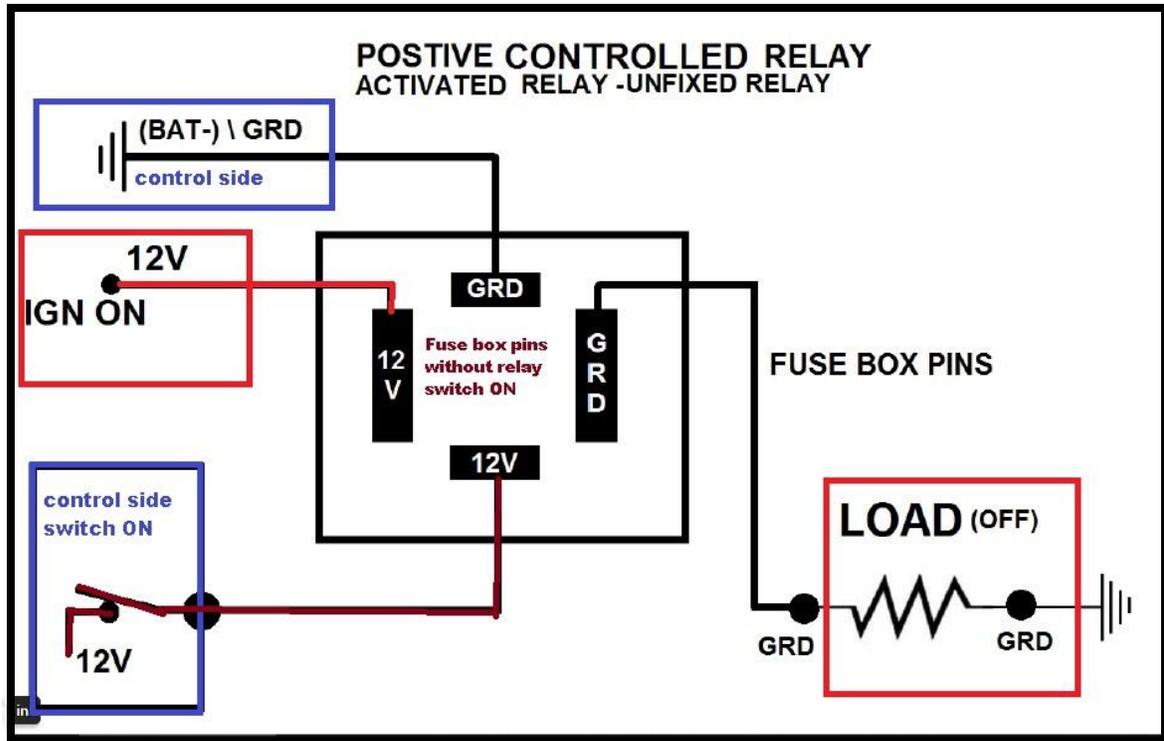

1.11- Don't blow your PCM

VIDEOS LINK


<https://schrodingersboxqm.com/how-to-test-wires-at-the-pcm/>

<https://schrodingersboxqm.com/dont-blow-your-pcm-part-1/>

<https://schrodingersboxqm.com/dont-blow-your-pcm-part-2-2/>

<https://schrodingersboxqm.com/dont-blow-your-pcm-part-2/>
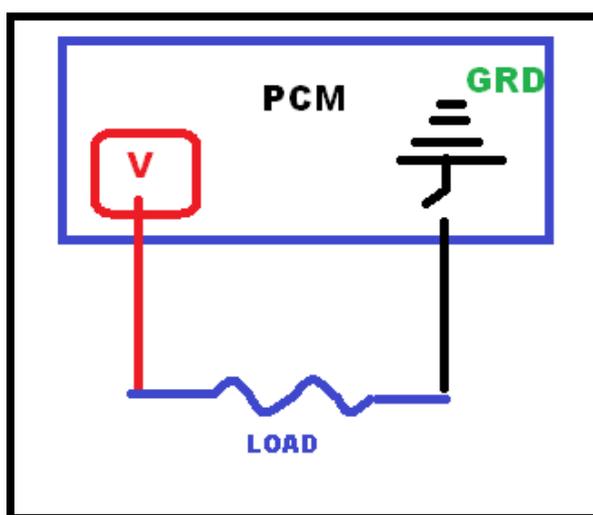
<https://schrodingersboxqm.com/dont-fry-your-pcm-final-exam/>



LOAD

SOLENOIDS
LIGHTS
RESISTORS
COILS
MOTORS

NOT LOADS

SWITCHES
FUSES
JUMPER WIRES
TRANSISTORS
PCM

IMPORTANT RULES

RULE 1:

- Always needs to be a load in a circuit! If there is no load (no resistance) then you have a short circuit.

Rule 2 :

- DVOM in volts mode is almost always safe.
- Amp clamps are available for DVOM and are always safe

Rule 3 :

- DVOM continuity tests are almost always safe.
- It isn't safe if we exceed the amount of amperage that the circuit can tolerate.

Rule 4 :

- Led test lights are virtually fail-safe but incandescent ones should be used with caution. An incandescent test light draws 250mA. A LED test light draws only 50mA. If in doubt, use an LED. But Incandescent lights can be useful if you want to operate a circuit with low amperage.

Rule 5 :

- 5v. circuits are generally safe.
- 5v. circuits wires are thin wires
- Sensor signal wires can tolerate up to 5v.

Rule 6 :

- 12v. circuits are always orange flags.
-

Rule 7:

- DVOM in amps mode should be used with extreme caution
It's potentially very dangerous to PCM since causing a short circuit on a PCM controlled switch (transistor) will likely blow it!!!

Rule 8


- Jumper wires are only used on the same side of a circuit (In Series) to bypass a switch or an open. Never jumper positive to negative without a load (such as test light)- ever!!!

Rule 9:

- Never replace a bad PCM until you find out what caused it.

Rule 10

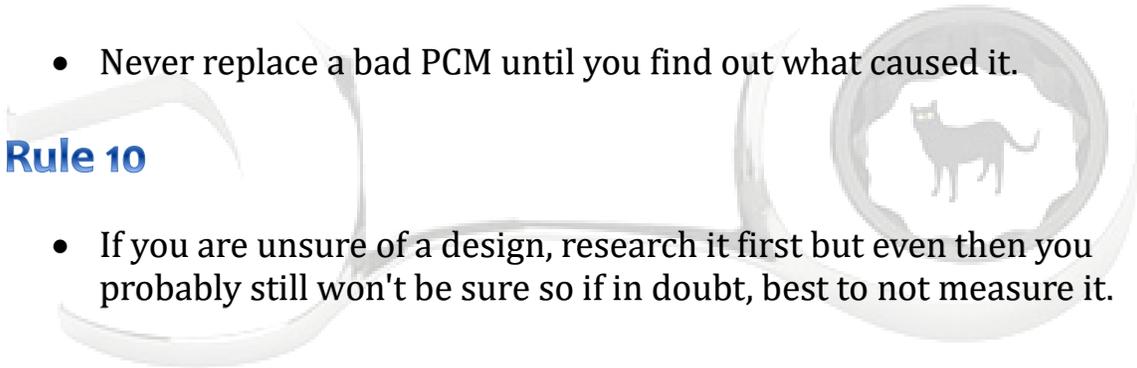- If you are unsure of a design, research it first but even then you probably still won't be sure so if in doubt, best to not measure it.



Schrodingers Box

SECTION 2

WIRING DIAGRAM TUTORIAL

VIDEOS LINK

<https://schrodingersboxqm.com/wiring-diagram-tutorial-part-1/>

<https://schrodingersboxqm.com/wiring-diagram-tutorial-part-2/>

<https://schrodingersboxqm.com/wiring-diagram-tutorial-part-3/>

<https://schrodingersboxqm.com/wiring-diagram-tutorial-pt-4-case-study/>

- Begin with the load you suspected then go back step by step
- Mostly power sources in the top and ground in the bottom
- You may find lines that go to the end of the page, on the next page you same lines with the numbering.
- Diagram always at rest state, all switches off except some devices are power all time like alarm system and clock
- The dotted box indicates that there are other components in this box that haven't appeared on this page.
- **Load devices must be controlled by a power source or by the ground.**
- **The most common PCM controls the ground of the relay, and then the relay controls load devices.**
- **Colors codes**







BLACK	BLK	BK	B	PINK	PNK	PK	K
BLUE	BLU	BU	U	PURPLE	PPL	PL	P
BROWN	BRN	BN	N	RED	RED	RD	R
CLEAR	CLR	CR	L	TAN	TAN	TN	-
DARK BLUE	DK BLU	DK BU	DB	VIOLET	VIO	VI	-
DARK GREEN	DK GRN	DK GN	DG	WHITE	WHT	WT	W
GREEN	GRN	GN	G	YELLOW	YEL	YL	Y
GRAY	GRY	GY	S	GROUND	GND	GN	G
LIGHT BLUE	LT BLUE	LT BU	-	CONNECTOR			C
LIGHT GREEN	LT GRN	LT GN	-	REFERENCE	REF		
ORANGE	ORG	OG	O	SKY BLUE		SB	















BLUE / BLACK	L/B	YELLOW / GREEN	Y/G
RED / WHITE	R/W	BLACK / WHITE	B/W
RED / YELLOW	R/Y	WHITE / GREEN	W/G
BLUE / YELLOW	L/Y	WHITE / RED	W/R
BLUE / GREEN	L/G	GREEN / YELLOW	G/Y
BLUE / WHITE	L/W	YELLOW / RED	Y/R
BROWN / WHITE	BR/W	YELLOW / BLACK	Y/B

• Ground locations codes


G 1--	FRONT CAR	G 7--	LEFT REAR DOOR
G 2--	INSTRUMENTAL PANEL	G 8--	RIGHT REAR DOOR
G 3--	PASSENGER SIDE	G 9--	ROOF
G 3--	B CENTER PILLAR	G 9--	A FRONT PILLAR
G 4--	REAR CAR	G 9--	C REAR PILLAR
G 5--	LEFT FRONT DOOR		
G 6--	RIGHT FRONT DOOR		

• Symbols

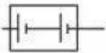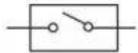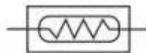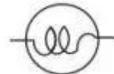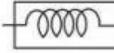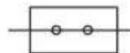
			
Battery	Open Switch	Motor	Sensor
			
Ground	connection	Light	Solenoid
			
Fuse	No Connection	Transistor	Capacitor
			
Closed Switch	Connector	Variable Resistor	Diode
			
Circuit Breaker	Thermo Switch	Resistor	Zenor Diode

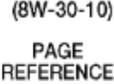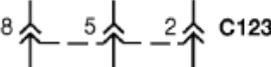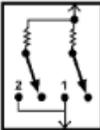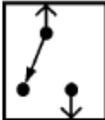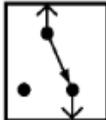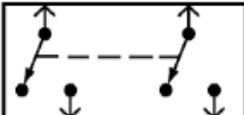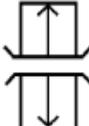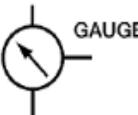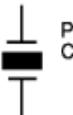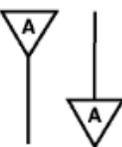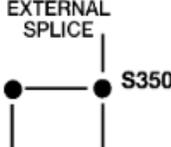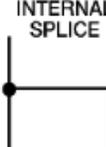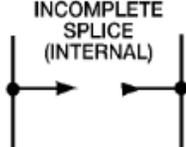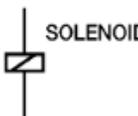 FUSIBLE LINK  FUSE  CIRCUIT BREAKER OR PTC PROTECTION DEVICE	 BATTERY  IN-LINE CONNECTORS 2 C123 2 C123
 BATT A0 HOT BAR  CHOICE BRACKET  (8W-30-10) PAGE REFERENCE	 MULTIPLE CONNECTOR 8 C123 5 C123 2 C123  MALE CONNECTOR 4 C1  FEMALE CONNECTOR 6 C3
 CLOCKSPRING  GROUND G101  SCREW TERMINAL	 SINGLE FILAMENT LAMP  DUAL FILAMENT LAMP  ANTENNA
 RESISTIVE MULTIPLEX SWITCH	 NPN TRANSISTOR  PNP TRANSISTOR  TONE GENERATOR
 OPEN SWITCH  CLOSED SWITCH	 LED  PHOTODIODE  DIODE  ZENER DIODE
 GANGED SWITCH  SLIDING DOOR CONTACT	 OXYGEN SENSOR  GAUGE  PIEZOELECTRIC CELL
 WIRE ORIGIN & DESTINATION SHOWN WITHIN CELL  WIRE DESTINATION SHOWN IN ANOTHER CELL	 RESISTOR  POTENTIOMETER  VARIABLE RESISTOR OR THERMISTOR  HEATER ELEMENT
 EXTERNAL SPLICE S350  INTERNAL SPLICE  INCOMPLETE SPLICE (INTERNAL)	 NON-POLARIZED CAPACITOR  POLARIZED CAPACITOR  VARIABLE CAPACITOR
 ONE SPEED MOTOR  TWO SPEED MOTOR  REVERSIBLE MOTOR	 COIL  SOLENOID  SOLENOID VALVE

CIRCUIT SYMBOLS

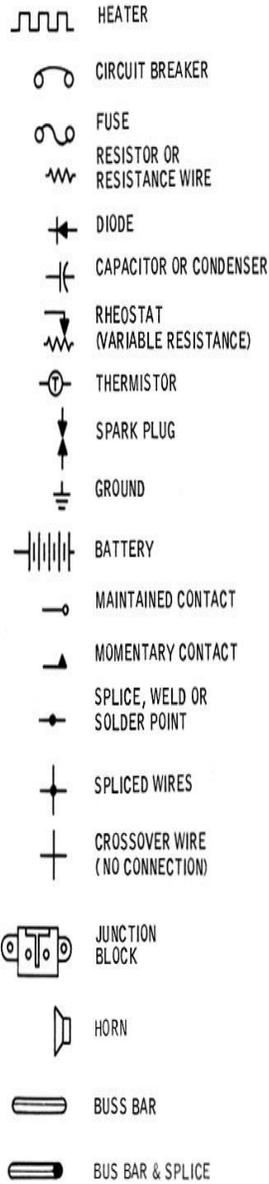


SWITCHES

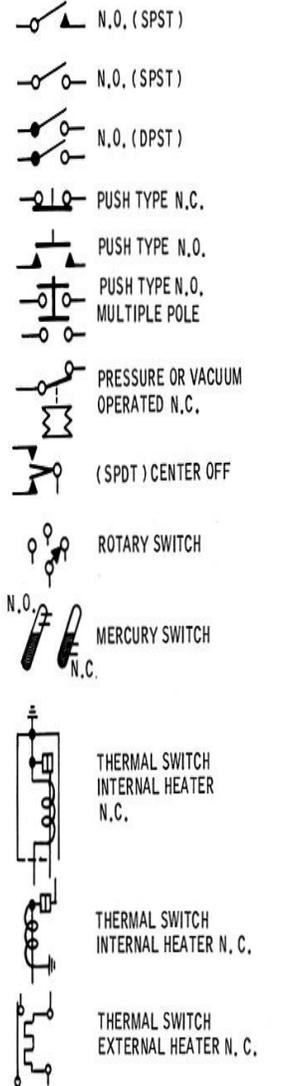


N.O. - NORMALLY OPEN
 N.C. - NORMALLY CLOSED
 S.P.S.T. - SINGLE POLE, SINGLE THROW
 D.P.S.T. - DOUBLE POLE, SINGLE THROW
 S.P.D.T. - SINGLE POLE, DOUBLE THROW
 D.P.D.T. - DOUBLE POLE, DOUBLE THROW


RELAYS

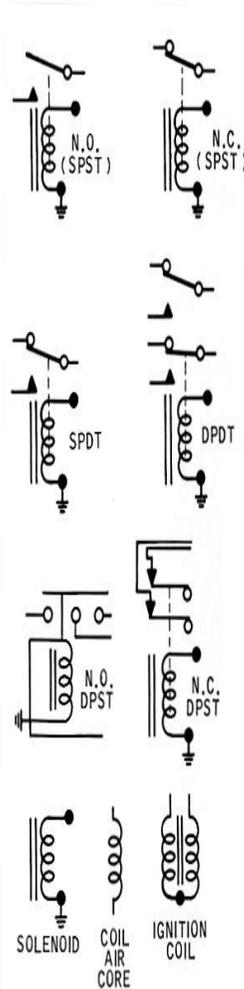

LAMPS

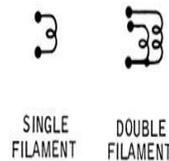

MOTORS

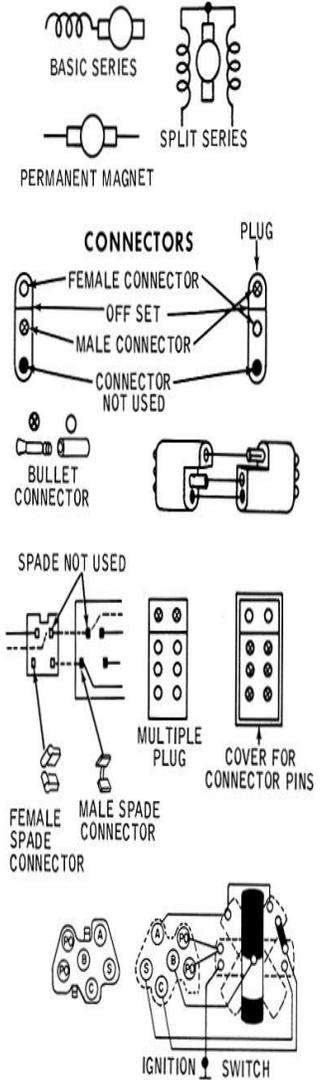

~ AND/OR * WIRE FUNCTION NOT APPLICABLE TO THIS CIRCUIT
 (14), (16) ETC. ALL NUMBERS IN PARENTHESIS () INDICATE WIRE GAGES
 (A), (B), ETC. ALL LETTERS CIRCLED INDICATE CONNECTION LOCATION.
 ★ TO POWER SOURCE

SECTION 3

ENGINE SENSORS

3.1- Mass air flow sensor (MAF)


VIDEOS LINK

<https://www.youtube.com/watch?v=MHsfAXog-FI&t=14s>

<https://www.youtube.com/watch?v=zxMxPH5jQmw&t=13s>

Detect the amount of air entering the engine by Measuring air Flow (gram/second)

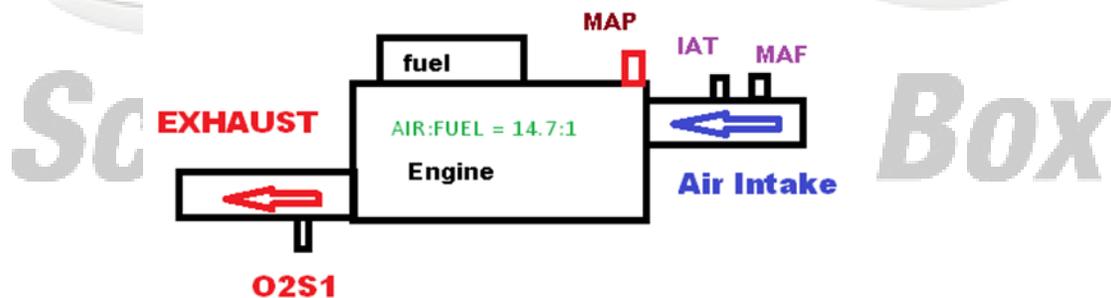- Idle = 2 to 7 g/s
- RPM 2500 = 15 to 25 g/s
- Most models have IAT (Intake air temp sensor) integrated within.



- PCM controls the temperature of the wire by holding the wire at a constant temperature above ambient temperature.
- More air enters leads to a decreased temperature of the wire
- PCM detects changes in current to measure airflow



- **Hotwire MAF sensors have two types :**

1- **Analogue** = 0 v. To 5 v.

Air \uparrow \rightarrow voltage \uparrow WOT = 5 V.

2- **Digital** = 2000 Hz to 6000 Hz

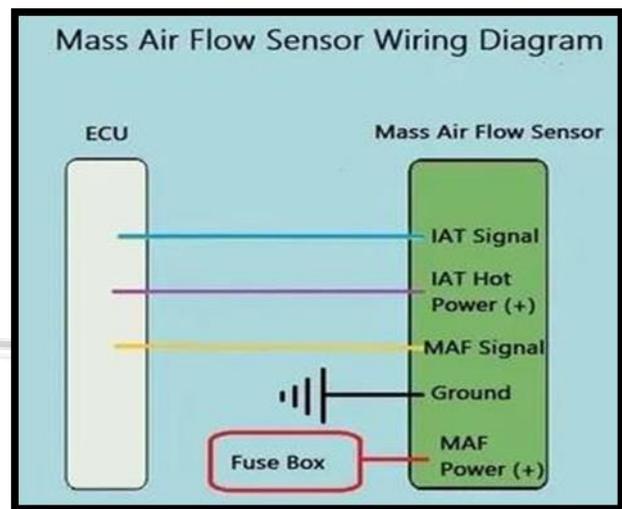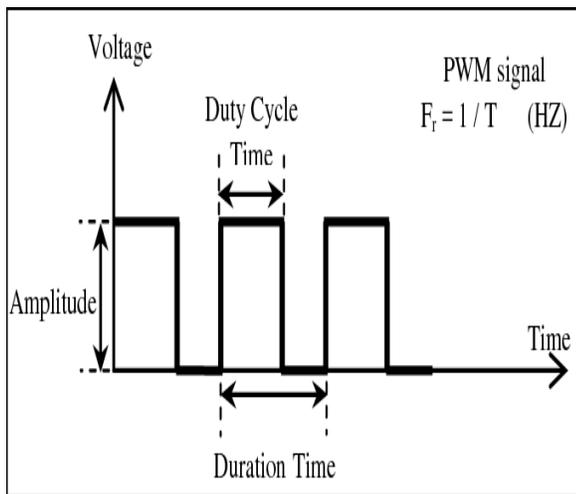- **Measure frequency of change in Volt. from 0 to 5 V (Duty cycle time)**




COMMON MAF SENSOR FAULT CODES

- **MAF circuit malfunction: P0100**
- **MAF circuit range/performance: P0101**
- **MAF circuit low input: P0102**
- **MAF circuit high input: P0103**
- **MAF circuit intermittent P0104**
- **MAF sensor a faulty or contaminated: P0171**

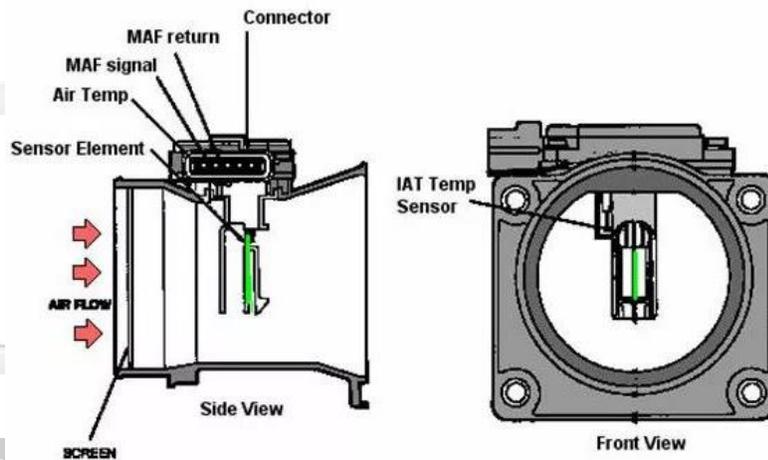3.2- Intake Air Temp Sensor (IAT)

- Video link <https://www.youtube.com/watch?v=1pOGSCsU-T8>
- Can be tested on the bench by applying heat and measuring the change in resistance As temp increased Resistance decreased
- Can test signal wire for Voltage from 0v. To 5v.
- Temperature $\uparrow \rightarrow R \downarrow \rightarrow V \uparrow$
- Some models have MAF integrated within
- 3 WIRE SENSOR



COMMON IAT SENSOR FAULT CODES

- P0110 Intake Air Temperature Circuit Malfunction Bank 1
- P0111 Intake Air Temperature Circuit Range/Performance Problem Bank 1
- P0112 Intake Air Temperature Circuit Low Input Bank 1
- P0113 Intake Air Temperature Circuit High Input Bank 1
- P0114 Intake Air Temperature Circuit Intermittent Bank 1



3.3- Throttle Position Sensor (TPS)

VIDEOS LINK


<https://www.youtube.com/watch?v=FJjobCD6y8fk&t=14s>

<https://www.youtube.com/watch?v=wP1CF4p8FGs>

- Used to monitor the air intake of an engine. The sensor is usually located on the butterfly spindle/shaft so that it can directly monitor the position of the throttle.
- Measures angle of the throttle shaft
- More openness leads to more Air leads to more volt.
- Can be tested on the bench by rotating it and measuring the change in resistance between signal & 5v. Reference wire
- Can test signal wire Voltage from 0.5v to 4.5v

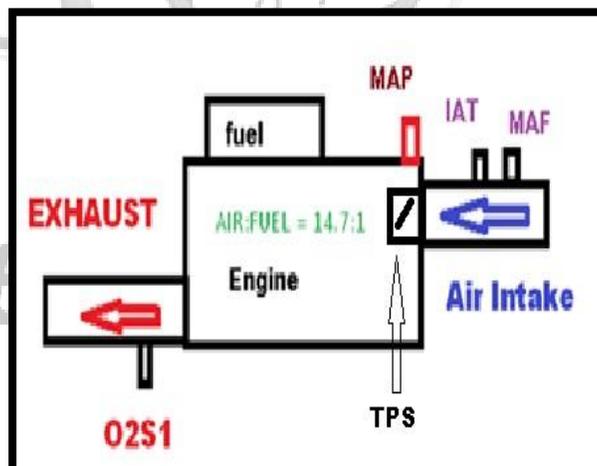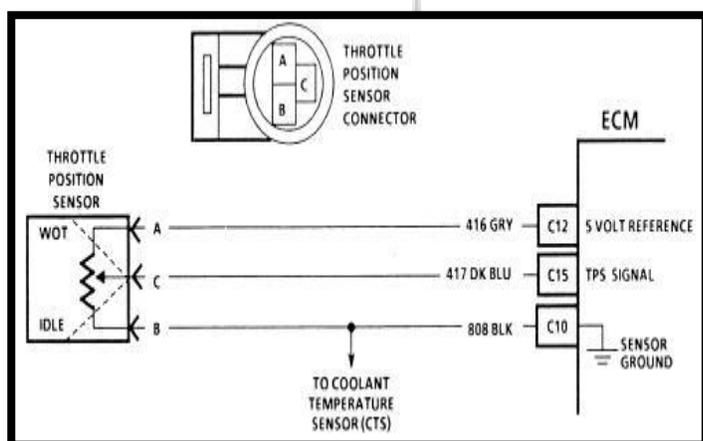

TPS VOLTAGE CHECKS

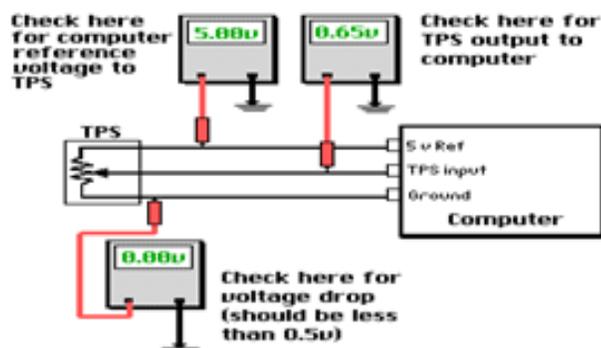



3.4- Manifold Absolute Pressure Sensor (MAP)

VIDEOS LINK

<https://www.youtube.com/watch?v=xutynSVO0xl>

<https://www.youtube.com/watch?v=mLOB-l6WP6s>

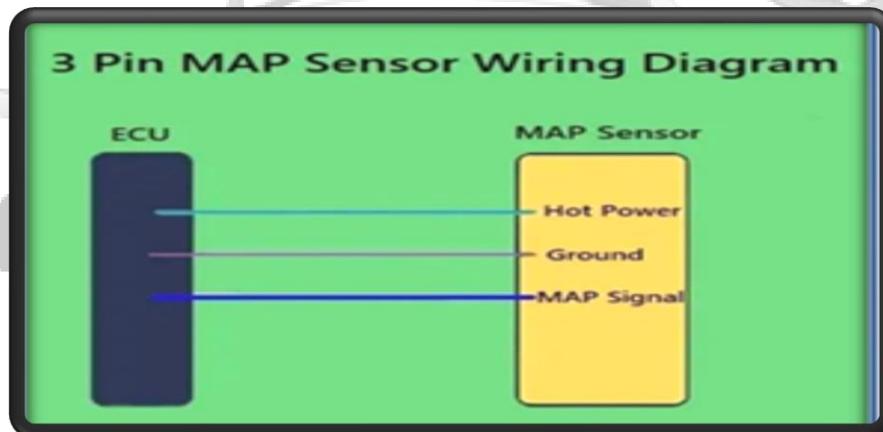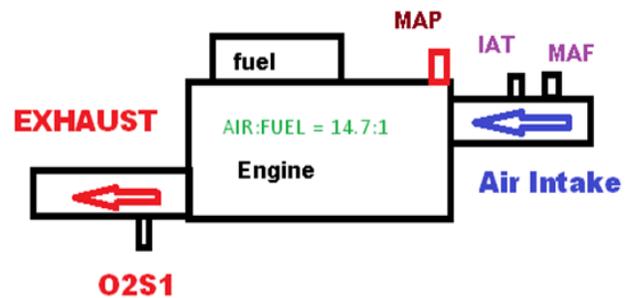- Measures manifold intake air pressure
- Range from 1 v to 5 v
- Idle = 1.5 v
- Increasing **RPM** leads to increasing **Air intake** so increases **volt** reading




3.5- Oxygen up Stream Sensor (O2S1)


Videos link

<https://www.youtube.com/watch?v=XOYDwIWS6Ho>
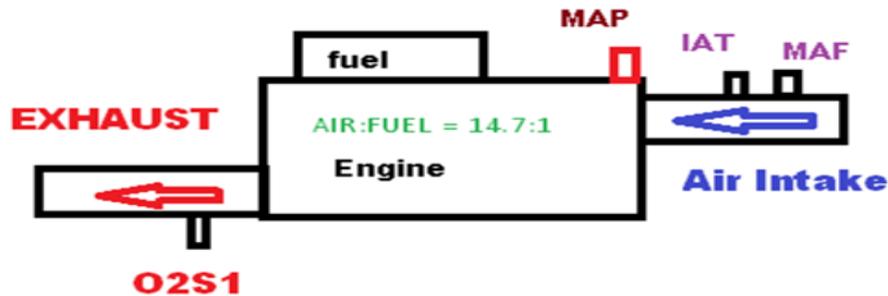
<https://www.youtube.com/watch?v=K8GLH6ubXoc>




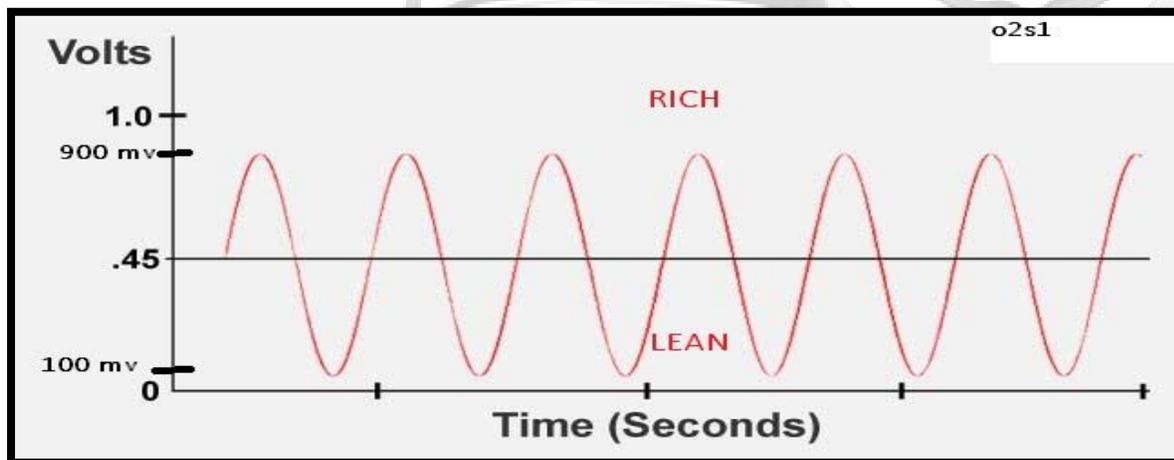
- Detect oxygen & hydrocarbons in exhaust then send a voltage signal to PCM for control STFT & LTFT % to control AIR FUEL RATIO
- SIGNAL from 0.1 volt to 0.9 volt



- PCM oscillates reading from o2s1 between 100mv. and 900mv. give waveform reading
- If the engine is at a stoichiometric ratio it must be oscillating between 100mv. & 900mv
- Above 450 mv. It is a rich condition
- Below 450mv. It is a lean condition

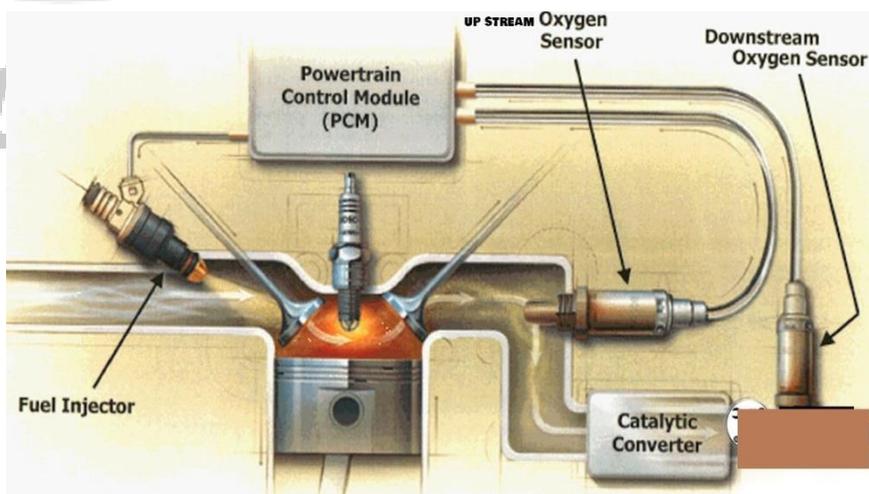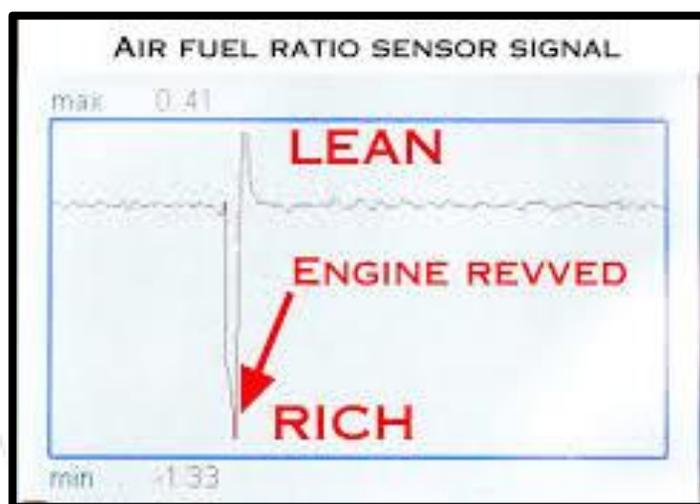3.6- Air fuel ratio sensor (A/F SENSOR)

- Detect Air: Fuel ratio in exhaust then send current (Amperage) signal to PCM for control LTFT & STFT
- Signal from -1.33 (mA) To + 0.41 (mA)



3.7- Knock Sensor (KS)

Videos link


<https://schrodingersboxqm.com/knock-sensors-diagnosis-and-understanding-part-1/>

<https://schrodingersboxqm.com/knock-sensors-diagnosis-and-understanding-part-2/>


- “Knocking” occurs when the air-fuel mixture self-ignites prematurely. Sustained knocking causes damage primarily to the cylinder head gasket and cylinder head.
- The knock sensor identifies the high-frequency engine vibrations characteristic of knocking and transmits a signal to the PCM
- PCM controls ignition timing till knock disappeared

• Types of Knock Sensor

1. Broadband

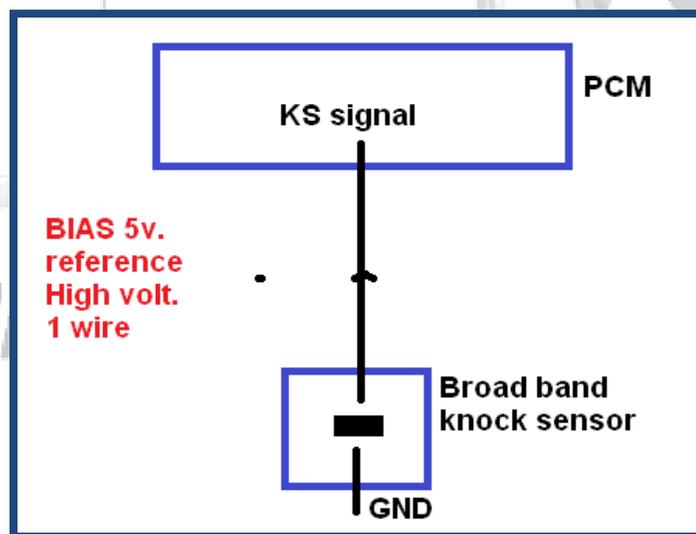

2 - Flat response

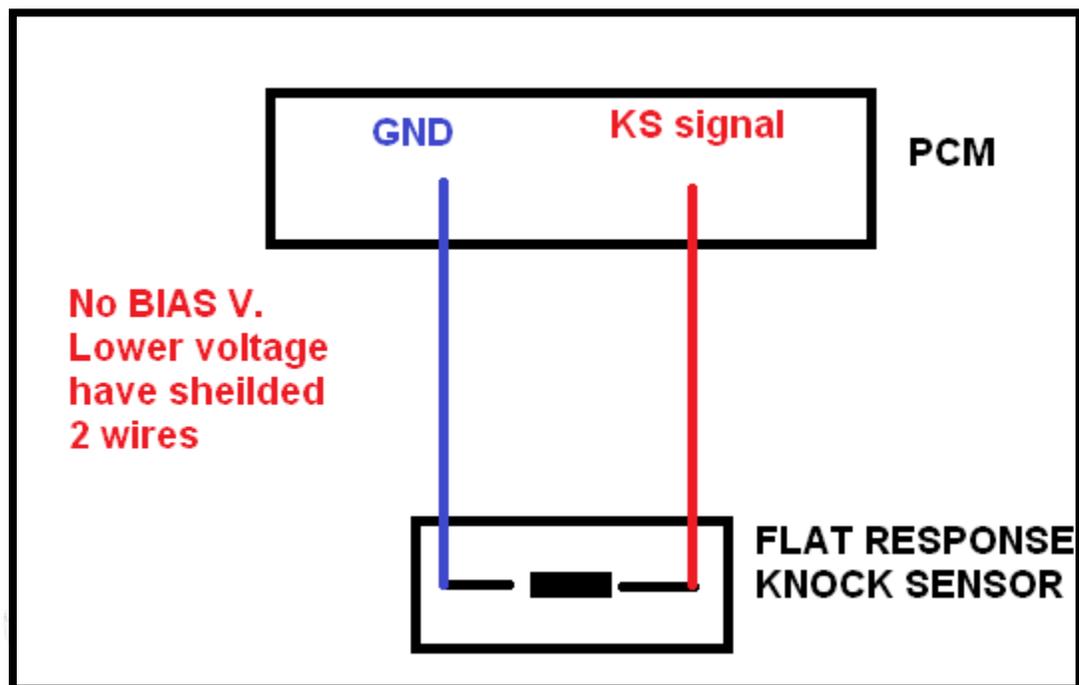

3.8 – Engine coolant temperature sensor (CTS) (ECT)

Videos link

<https://schrodingersboxgm.com/diagnosis-and-understanding-coolant-temp-sensor-part-1/>


<https://schrodingersboxgm.com/diagnosis-and-understanding-coolant-temp-sensor-part-2/>

- **FUNCTION :**

1. Reports engine temperature to PCM
2. Fan control
3. Temperature gauge
4. Important for Spark to advance control
5. Important for Secondary Air Injection System (open\closed loop status)

- **FAILURE SYMPTOMS :**

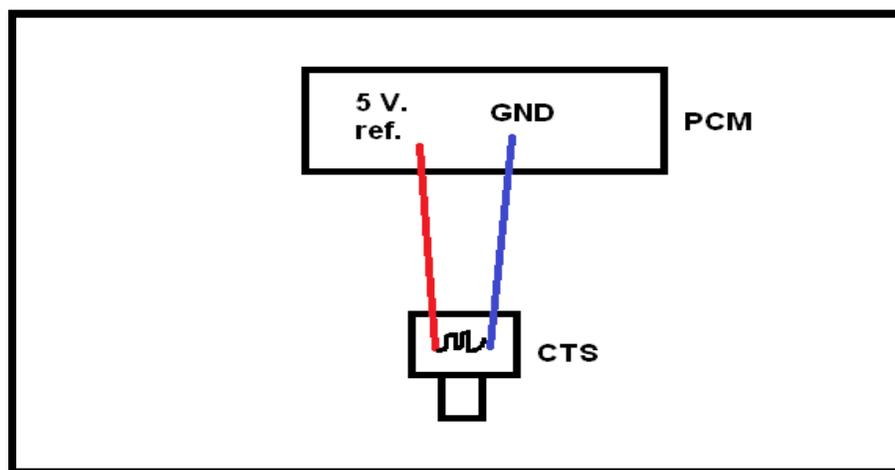1. Irrational fan control (over cooling \ heating)
 2. Failure to enter closed loop.
 3. Poor fuel economy (rich)
 4. DTC
 5. Inaccurate temperature gauge reading
- PCM detects voltage drop in a circuit to calculate the temperature
 - Thermistors work by negative temperature coefficient
 - When Temp. increased, the resistance decreased led to voltage drop decreased




3.9 - Camshaft position sensor (CPS) Crankshaft position sensor (CKPS)

Videos link

<https://schrodingersboxgm.com/cam-and-crank-sensor-basics-part-1/>

<https://schrodingersboxgm.com/cam-and-crank-sensor-basics-part-2/>


A- The camshaft position sensor

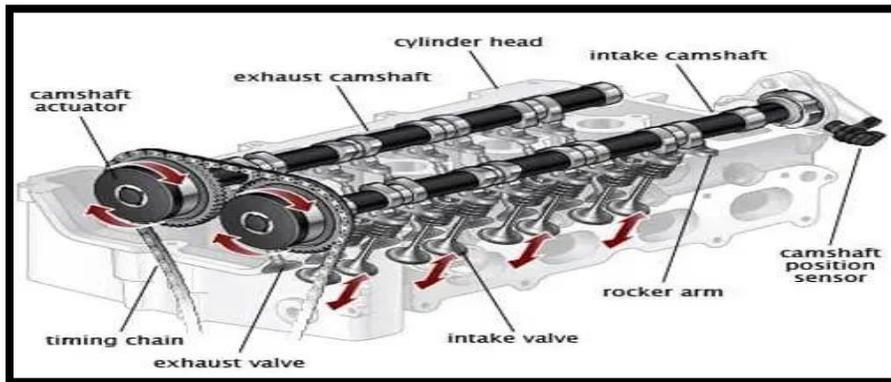

- It determines the location of the camshaft and its angle to determine the position of the engine cylinder's piston to be operated.
- To produce the spark when the piston is at the top dead center
- To determine the duration of the injection pulse
- To know the firing order of the engine cylinder

B -Crankshaft position sensor (CKPS)

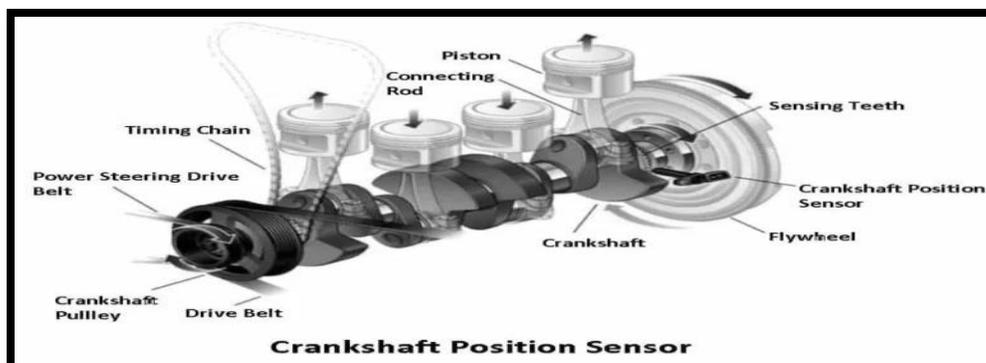- Measures the position of the crankshaft.
- It detects the crankshaft position and sends the signal PCM to calculate the injection timing, ignition timing, and engine RPM according to the crankshaft position sensor's signals.



TYPES OF CAMSHAFT & CRANKSHAFT POSITION SENSORS


1 - INDUCTIVE SENSOR


- This type of sensor is composed of a magnetic core and copper conductor winding mounted on an isolated coil that generates an AC voltage sending an alternating current signal to PCM
- 2 Wires sensor Same concept in wheel speed sensor (WSS)
- Continuity through sensor
- 5v or 12v to diagnose any open circuit

2 - HALL EFFECT SENSOR


- Hall-effect sensors generate a digital square wave signal instead of an analog AC signal.
- It consists of a three-pin connector (reference voltage, ground, and signal).
- Hall Effect sensors offer the advantage that they can detect static (non-variable) magnetic fields

TESTING BY OSCILLOSCOPE

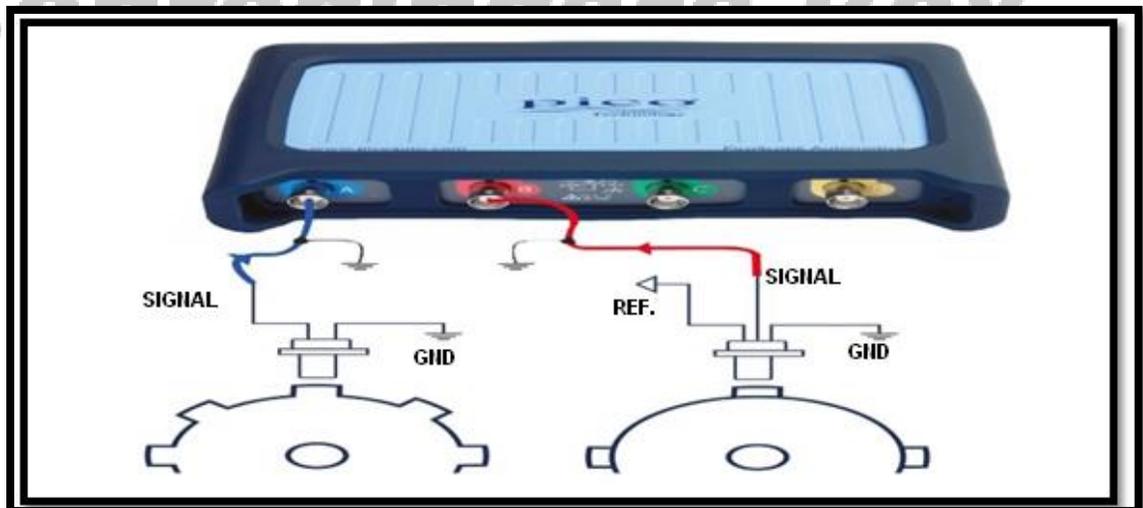

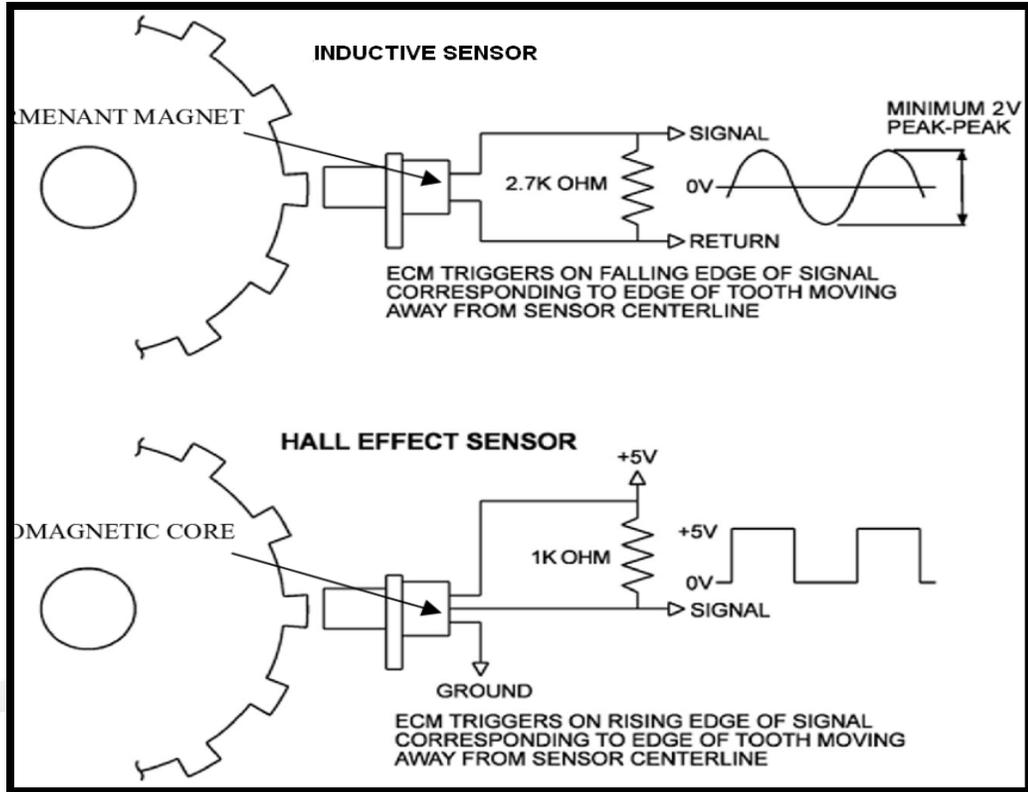

ENGINE SENSORS LOCATIONS

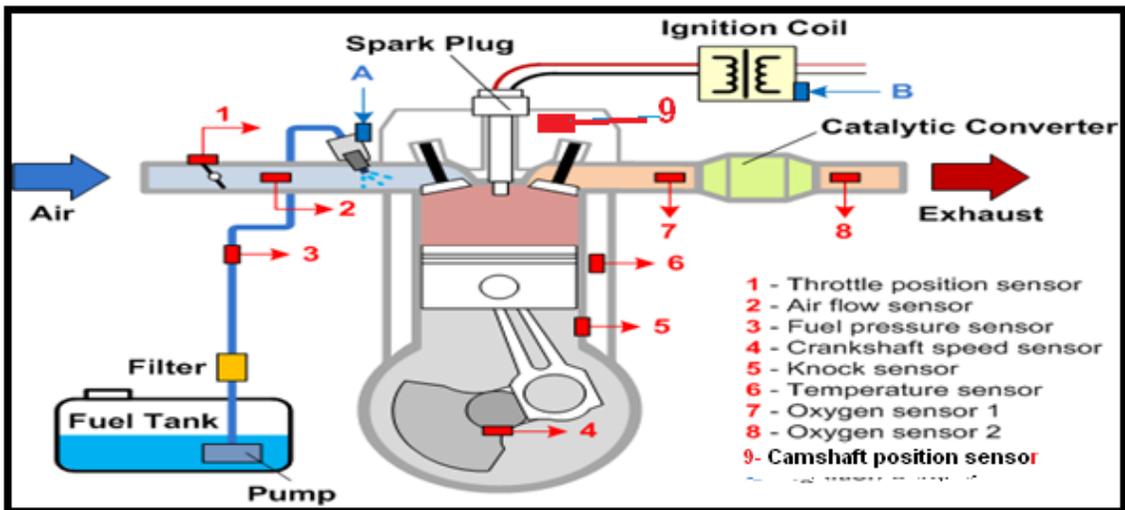


SECTION 4 FUEL TRIMS

Link to video

https://www.youtube.com/watch?v=5WnM_NsOtd8
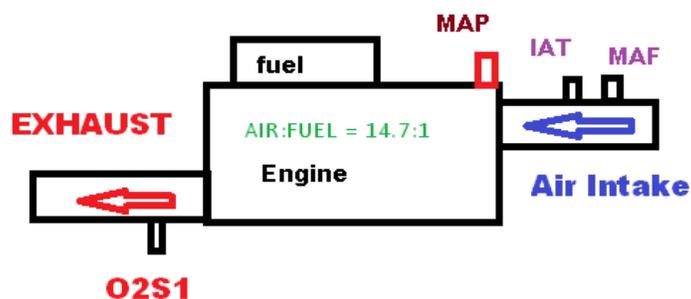
<https://www.youtube.com/watch?v=cAR00jZZ4Qc>



4.1 – fuel injection system

- **PCM** receives data from
 - MAF** (Mass airflow sensor
 - IAT** (Intake air temperature sensor)
 - MAP** (Manifold absolute pressure sensor)
 To detect how much air entered the engine
- **PCM** receives data from **O2S1** (Oxygen upstream sensor 1) or **A/F sensor** (Air fuel ratio sensor) to detect oxygen & hydrocarbons in the exhaust to adjust fuel trims
- The concept of fuel trims is identical in both **O2S1** & **A/F SENSOR**
- **O2S2** (Oxygen downstream sensor 2) to maintain the optimal activity of the catalytic converter
- stoichiometric ratio is Air : Fuel = 14.7 : 1 important for high performance & fuel economy
- **PCM** uses data from sensors to calculate the amount of fuel needed to be added to Stay in Stoichiometric Air Fuel
- Ratio by regulating pulse width of fuel injectors

4.2 -FUEL TRIMS definitions

Short-term fuel trim (STFT %)

Percentage of deviation from a normal amount of fuel added controlled by PCM to maintain stoichiometric ratio AFR

Long-term fuel trim (LTFT %)

Steady-state after the change in STFT % and become new state till a new change in STFT and change again to newer state and so on to keep stoichiometric ratio AFR

Normal range of LTFT & STFT is from -10% to +10%

DTC appeared if LTFT over +25% or less than -25%

4.3 - RELATION BETWEEN O2S1 & LTFT & STFT



In Case a Vacuum leak

⇒ Increase unmetered Air ⇒ Lean O2S1

⇒ +25% increase STFT to compensate for air from the leak

⇒ ↑ Fuel ⇒ ↑ LTFT ⇒ New steady state of LTFT at +25%

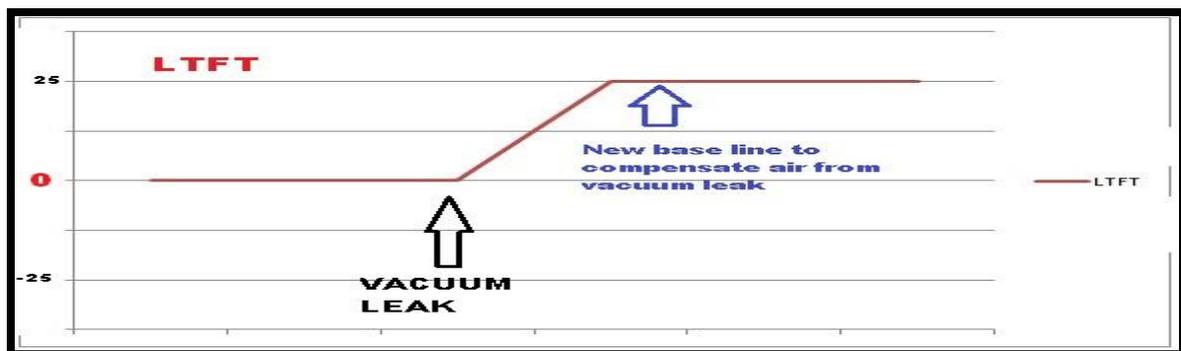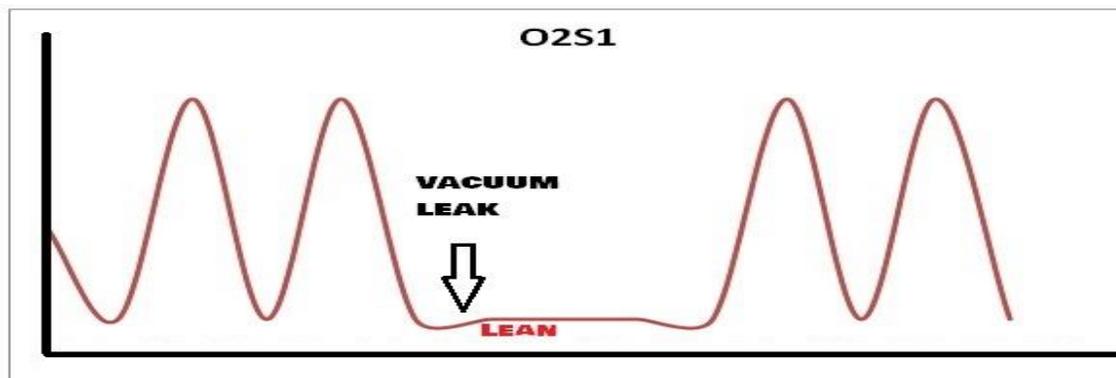⇒ Normal Air fuel ratio ⇒ normal O2S1 ⇒ normal STFT






Stop Vacuum leak

⇒ stop unmeasured Air ⇒ rich o2s1

⇒ -25% STFT decrease due to rich condition

⇒ ↓ Fuel ⇒ -25% LTFT ⇒ New steady state of LTFT at 0%

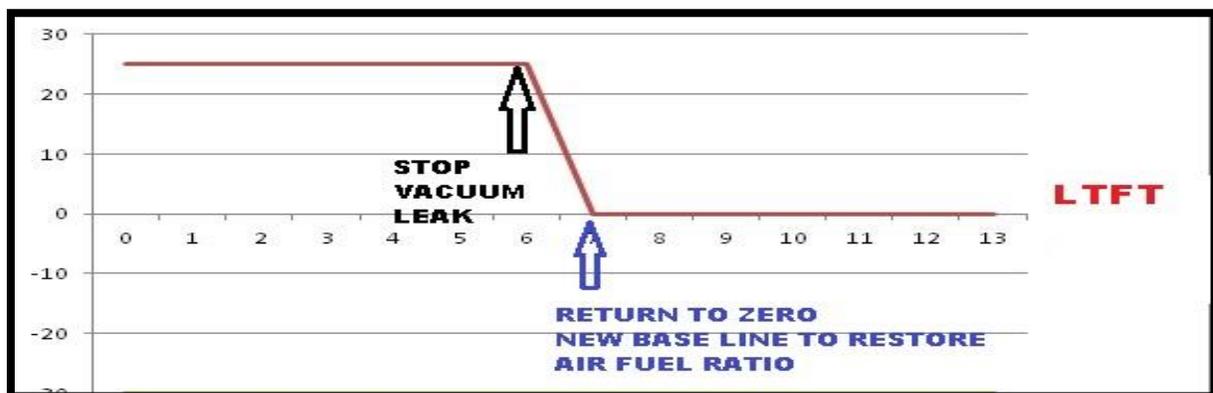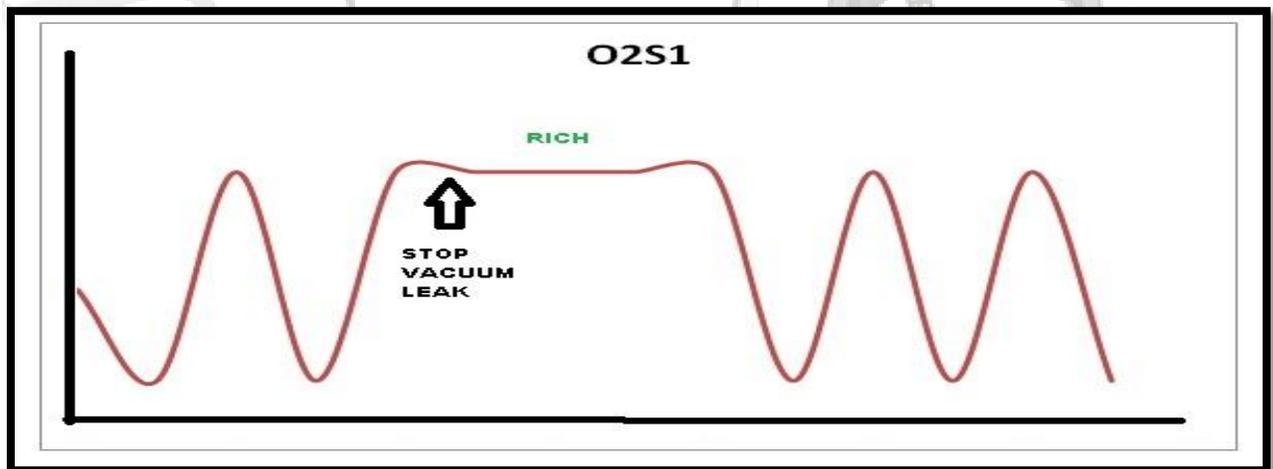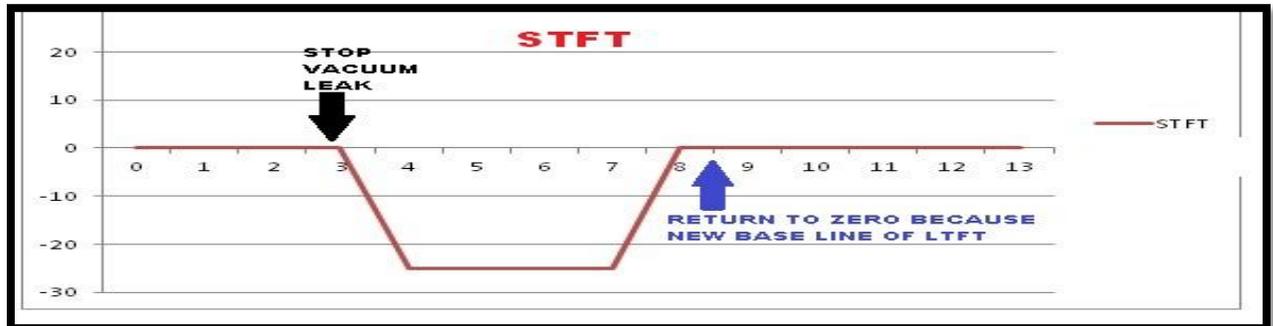⇒ Normal Air fuel ratio ⇒ normal O2S1 ⇒ normal STFT



4.5 - DIAGNOSIS BY O2S1 & LTFT & STFT

CODE P0171


Engine run lean bank1

- STFT = 0%
- LTFT = +25%
- O2S1 = 0.1 V.

CAUSES

A- AIR VACUUM LEAK

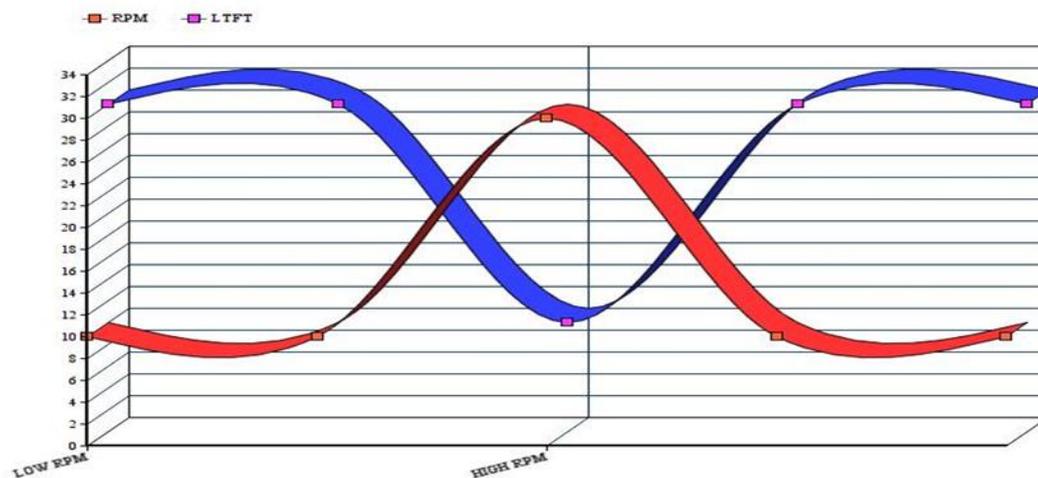
✿ BY $\uparrow\uparrow$ RPM \Rightarrow $\uparrow\uparrow$ Air intake \Rightarrow $\downarrow\downarrow$ % of unmetered air from leak to All air intake \Rightarrow $\downarrow\downarrow$ LTFT TO Normal value
If $\downarrow\downarrow$ RPM to IDLE \Rightarrow $\uparrow\uparrow$ LTFT again ✿



B- WEAK FUEL PUMP

✿ Increase RPM \Rightarrow More Need to fuel \Rightarrow increase LTFT to overcome the weakness of the fuel pump

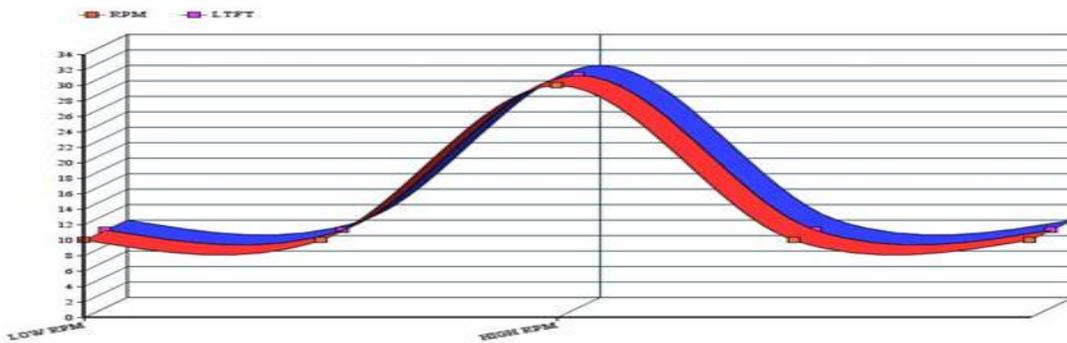✿ Test fuel pump pressure (normal range from 60 psi to 100 psi)



C- MAF DIRTY OR MALFUNCTION

Increase **RPM** = Increase unmetered Air intake = increase **LTFT**

CASE OF V ENGINE

- LTFT1 = +25% & LTFT2 = 0% \Rightarrow CAUSE IS VACUUM LEAK
- LTFT1 = +25% & LTFT2 = +25% \Rightarrow CAUSE MY BE ONE OF A or B or C